

UNIT - I

Hannan 219

### • PLC : Programmable Logic controller

A device which performs discrete or continuous logic in process plant or factory environment. It was developed originally to replace the relay.

#### Advantages



- Economy
- Small Physical size
- Suitable modular design
- High reliability
- Ease of Programming
- Rugged construction
- Ability to communicate with computer

These are used in area requiring micro-controller and PC both. Ground signal of sensor and ground signal to PLC are physically separated.

### • PLC Architecture
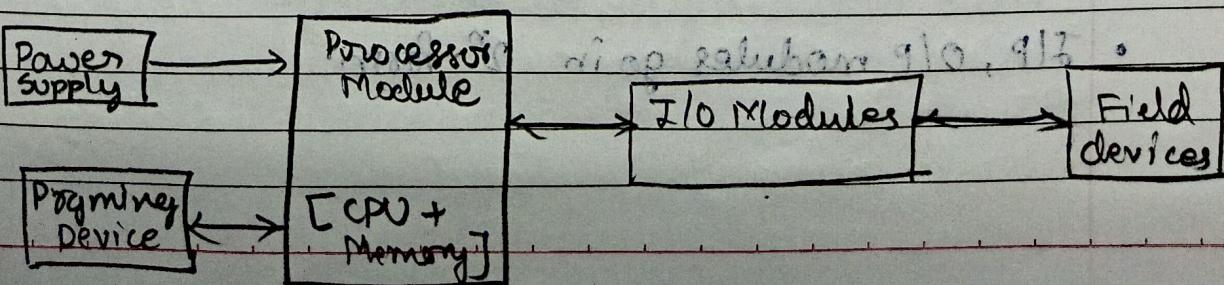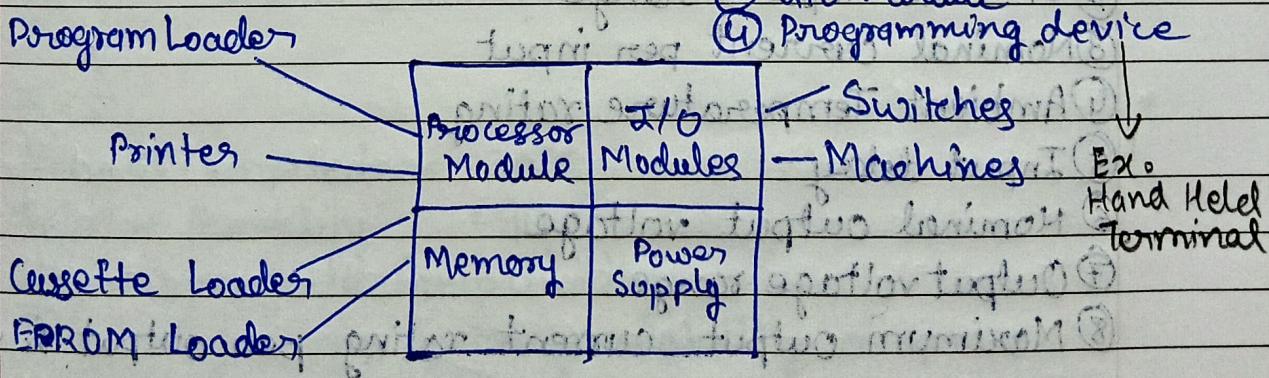
#### Basic Components :

- ① CPU and Memory Module
- ② Power Supply
- ③ I/O Module
- ④ Programming device



## • PLC Components

- ① I/O modules → 20 with analog input & output & digital input & output
- ② Power Supply → AC, DC
- ③ Peripheral → Handheld programmer, CRT programmer, Operator console
- ④ Conveyor belt → Limit switches.

## • Specs.

Max. of PLC operates  $\Rightarrow$  24VDC / 110VAC, 50Hz  
 Field Sensors.  $\Rightarrow$  4 to 20mA, 0 to 5V

Limitation of PLC is Programming [ladder diagram]

PLC  $\rightarrow$  24VDC or 110VDC, 50Hz  
 Field Sensors  $\rightarrow$  4 to 20mA, 0 to 5V

## • I/O specifications

- ① Nominal input Voltage
- ② On-state input V range
- ③ Nominal current per input
- ④ Ambient Temperature rating
- ⑤ Input delay
- ⑥ Nominal output voltage
- ⑦ Output voltage range
- ⑧ Maximum output current rating per output & module

• I/P, O/P modules go in 2" form

## Types of Control:-

- ① Temporal  $\rightarrow$  control based in time
- ② State  $\rightarrow$  control based in state level
- ③ Hybrid  $\rightarrow$  both temporal and state

DOMS

Page No.

Date / /

## • Typical specifications

No. of digital inputs = 120 [Generally  $2^n$ ]

↳ outputs = 64

No. of timers = 40

↳ auxiliary relays = 100

## Memory, Backup Storage

I/O Modules: 18 channels

Input devices to accept data [limit switches, relay contacts, push button, selector switches],

## • SCADA: Supervisory Control and Data Acquisition system

- ① Self diagnostic Function
- ② Space available [700 mm X 500 mm] - T899
- ③ PLC programming software.

MODBUS, HART, CAN protocols are used for communication in PLC to accept input data

Used in Industrial Sectors.

CAN protocol are used in automobiles.

TCP/IP serial communication.

## PLC=

Ambient Temperature =  $30^{\circ}\text{C}$

Relative Humidity = 90%

Electro-magnetic Compatibility


Warranty: 2 yrs with availability of spares

soft is guaranteed for 10 yrs.


drives, starters, relays, sensors, limit switches, etc.

long life & reliability mode

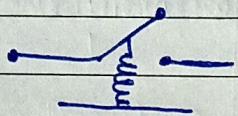
- switches → Has a spring  
push button → only one state; used for emergency start/stop
- switches : Output is Binary [0/1]



Non-locking

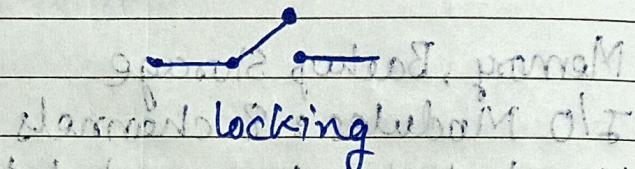

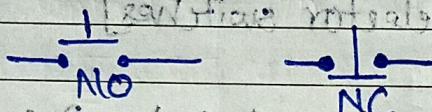Standard locking switch. When released, it returns to its initial position.



SPDT - Single pole double throw

DPST - Double pole single throw

Types: Basic, push-button, slide, thumbwheel, limit,


proximity, photoelectric, etc.

Rating: Current and Voltage depends on configuration of switch.
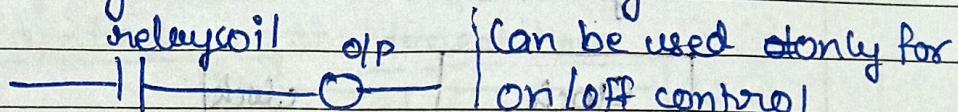
### • Input Module

- ① Input Module sense when a signal is received from a sensor on machine.
- ② Input Module converts input signal to correct voltage level for particular PLC.
- ③ Input Module isolates PLC from fluctuations in the input signal's voltage and current.
- ④ Input Module send a signal to PLC indicating which sensor originated the signal.

- Relays : switches whose operation is activated by an electromagnet is called a relay.



PWM → Pulse width modulation

Square wave with of same frequency with variable duty cycle.

- ## • Actuators


- ① Solenoid values
  - ② Lights

- ③ Motor Starters
  - ④ Servo Motors


- ## • Output Module

- ① It acts as a switch to supply power from the user power supply to operate the output
  - ② Output switching devices mostly often used to switch power to load in PLC.
  - ③ Relay for AC or DC load.
  - ④ Transistor for AC loads only.
  - ⑤ Transistors for DC loads only.

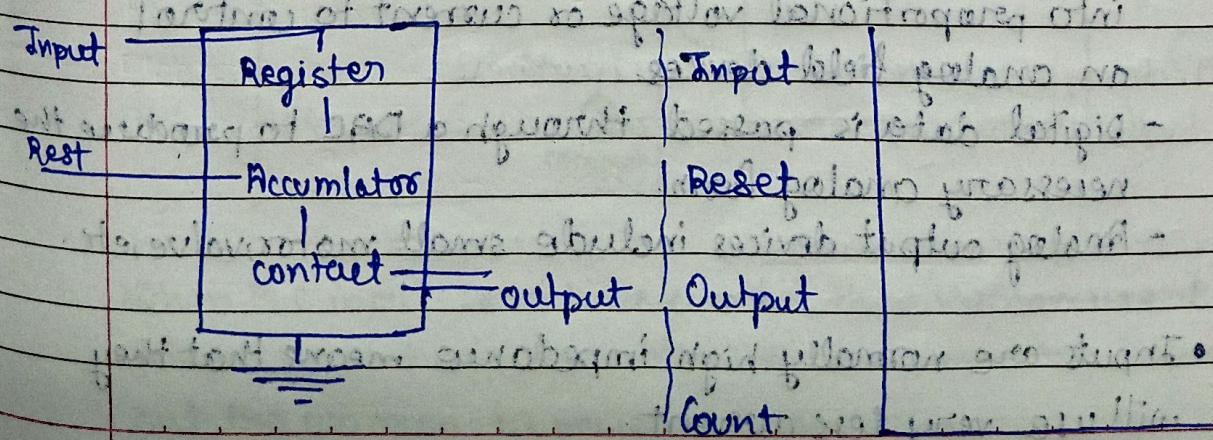- Counter : Digital counter output in form of a relay contact when a preassigned count value is reached



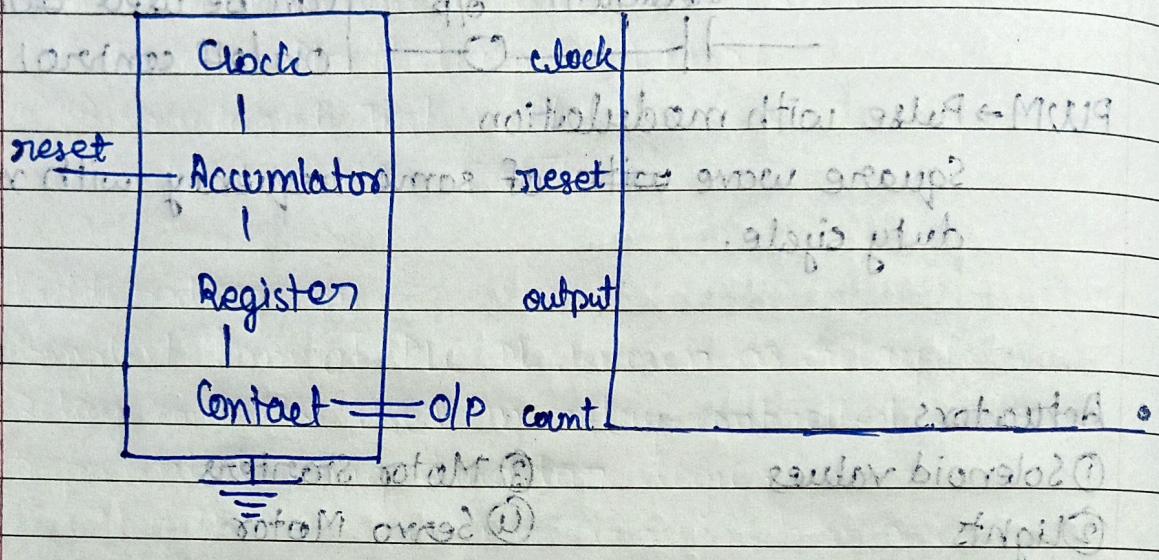- **Timer:** A timer consists of an internal clock, a count value register and an accumulator.



- **Analog Interface.**

### ① Analog Input Interface Module:

- It contains circuitry necessary to accept analog signals of voltage and currents from analog field devices.
- These signals are converted into digital value by ADC.
- Analog input sensing devices include temperature, light, speed, position transducer, etc.


### ② Analog Output Interface Module:

- Receives digital data from processor that is converted into proportional voltage or current to control an analog field device.
- Digital data is passed through a DAC to produce the necessary analog form.
- Analog output devices include small motor, valve, etc.

- Inputs are normally high impedance means that they will use very less current.

(NPN)

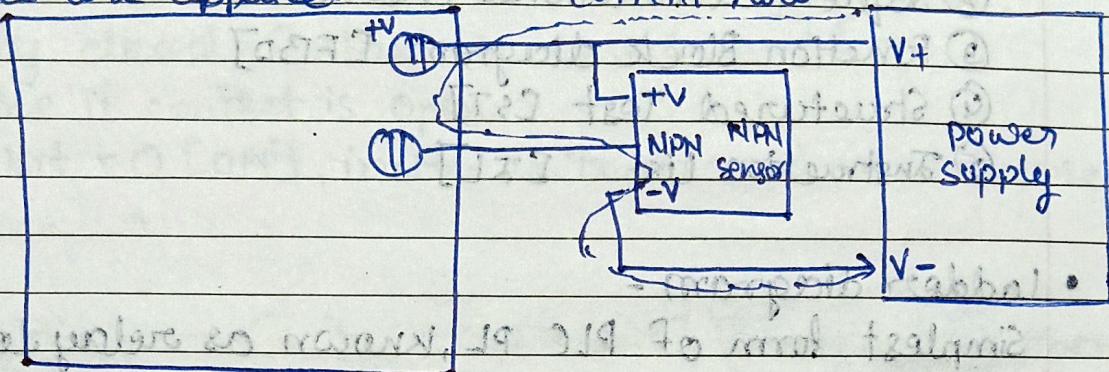- Sinking - When active, the output allows current to flow to a common ground. This is best selected when different voltages are applied.




When a PLC input card does not have a common but it has V+ instead, it can be used for NPN sensors. The current will flow out of card and we must switch to ground.

(PNP) → More popular than NPN

- Sourcing - When active, current flows from a supply, through output device and to ground. This method is best when all devices use a single voltage supply.

PLC input card for sourcing

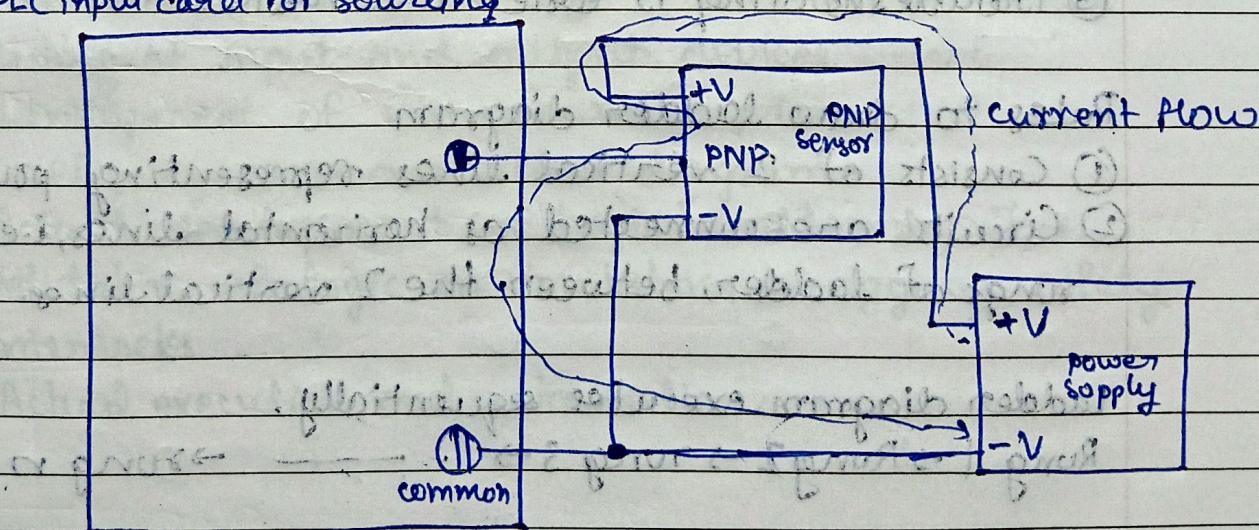

of high resistance to the bridge monitoring - 901

When PLC input card have common then we can use PNP sensors. Current will flow into the card and then through out the common to power supply.

- PLC Programming : 5, Most common are -

- (1) Ladder diagram [LD]
- (2) Sequential Function Charts [SFC]
- (3) Function Block Diagram [FBD]
- (4) Structured Text [ST]
- (5) Instruction List [IL]

- Ladder diagram -

Simplest form of PLC PL, known as relay logic.

Relay contacts used in relay-controlled systems are represented using ladder logic.

Function Block diagram is simple and graphical method to program multiple functions in PLC

Advantages of LD:

- (1) Easily programmed, easily understood PL.
- (2) Flexibility in programming and reprogramming.
- (3) Troubleshooting is easier and faster.

Rules to draw ladder diagram

- (1) Consists of 2 vertical lines representing power rails.
- (2) Circuits are connected as horizontal lines, i.e. the rungs of ladder, between the 2 vertical lines.

Ladder diagram executes sequentially.

Rung 1 → Rung 2 → Rung 3 → ... → Rung n

LDP - Basically symbolic set of instructions used to create controller.

3 fundamental symbols that are used to translate relay control logic to contact symbolic logic

Dot 5

Page No.

Date

/ /

① EXAMINE IF CLOSED

② EXAMINE IF OPEN

③ OUTPUT ENERGY

- Normally open: Contact is open  $\rightarrow E$

Examine if contact is closed.

Status bit = 1 [ON], instr. is True; & vice versa.


- Normally closed: Contact is closed  $\rightarrow \bar{E}$

Examine if contact is open.

Status bit = 0 [OFF], instr. is True & vice versa.

- Relay coil  $\rightarrow C$  [Output] if rung is TRUE, then ON

- Example

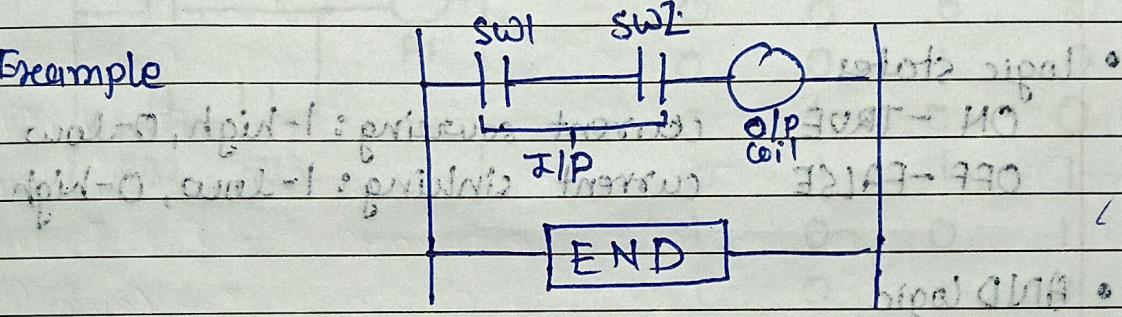

- Seven steps for development and implementation of logic

① Development of Block diagram or P&ID [Piping and instrumentation diagram]

② Listing of input and output devices.

③ Development of flow chart of process.

④ Developing cause and effect diagram

⑤ Actual development of logic [ladder logic]

⑥ Validation of logic on simulators; debugging, safety interlocks

⑦ Actual execution and optimization.

## • PLC instructions

- ① Relay
- ② Timer and Counter
- ③ Program Control
- ④ Arithmetic [Also logical]
- ⑤ Data Manipulation
- ⑥ Data Transfer
- ⑦ Other, such as sequencers.

wave ppty:

Odd cycle

② Frequency

encoders O/P are pulse proportional to speed of motor

## • Logic states


ON - TRUE

(current sourcing: 1-high, 0-low)


OFF - FALSE

(current sinking: 1-low, 0-high)




## • AND logic

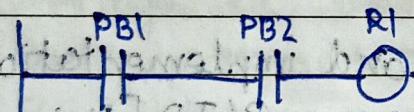

$$R1 = PB1 \text{ AND } PB2$$

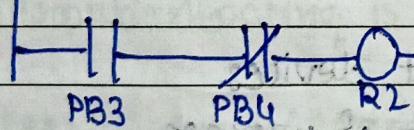


$$R2 = PB3 \text{ AND } PB4$$

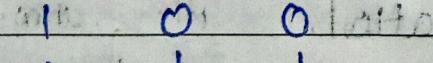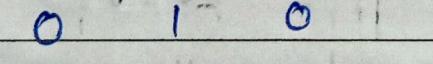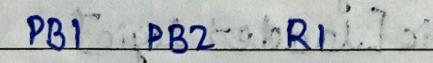

Switch - NO  $\rightarrow$  1 , NC  $\rightarrow$  0


- OR logic

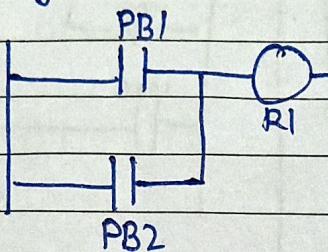

$$R1 = PB1 \vee PB2$$


PB1	PB2	R1
0	0	0
0	1	1
1	0	1
1	1	1

- Combined AND & OR logic


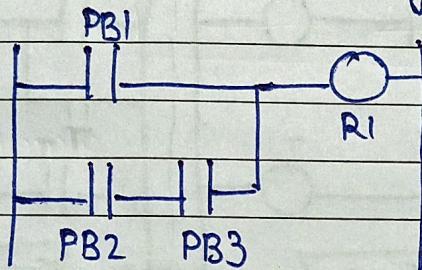


PB1	PB2	PB3	R1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

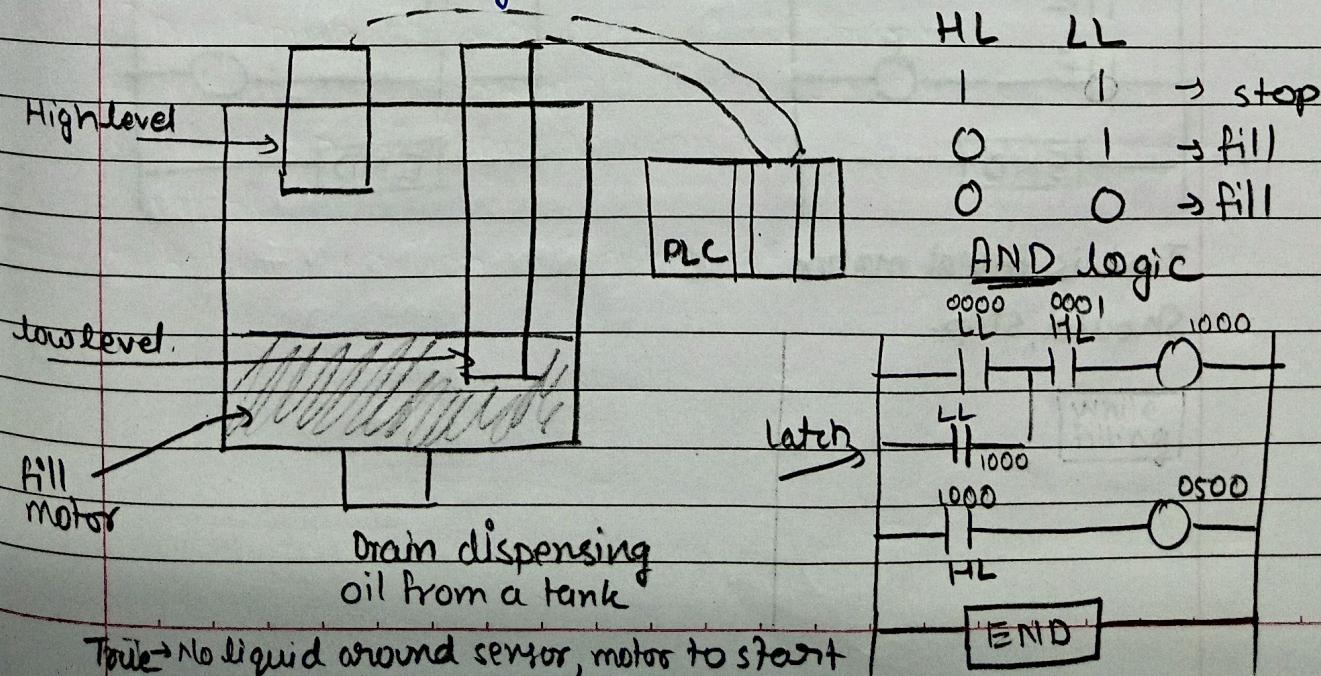
- Example - Oil is consumed randomly. The tank needs to be refilled by turning on a pump. 2 Hydrostatic switches are used to detect a high & low level.



When  
draining

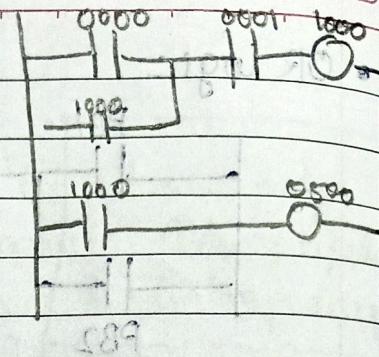
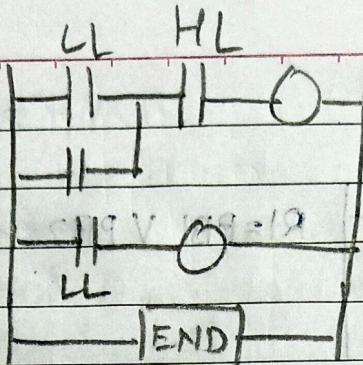


- While Filling

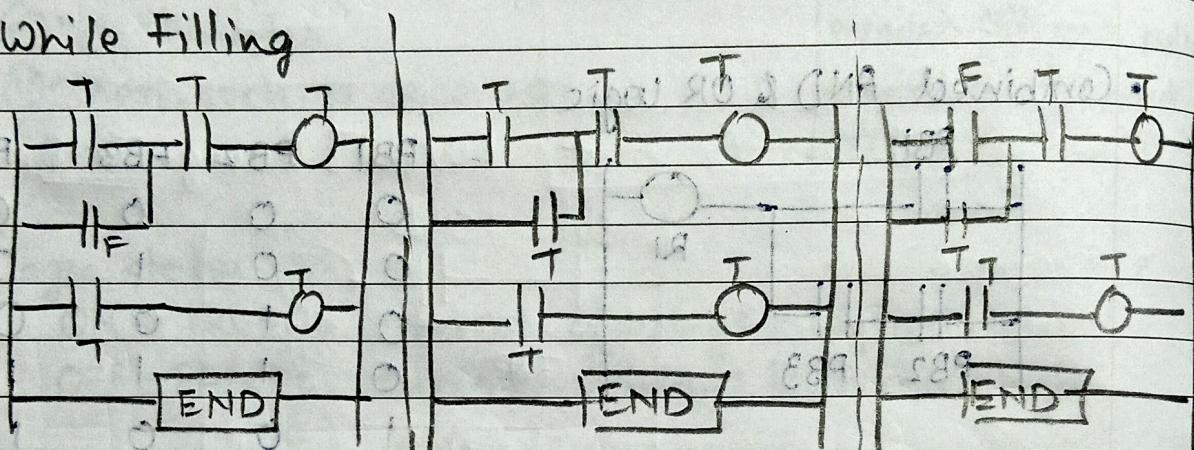

Tank is empty, motor  
is off.  
[LL switch is off]

Tank reaching high  
level.

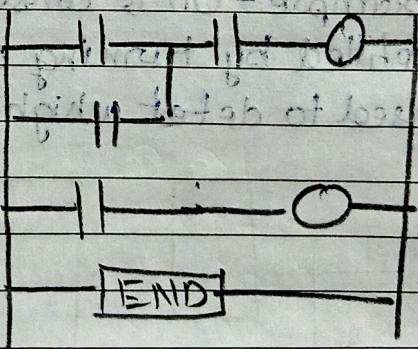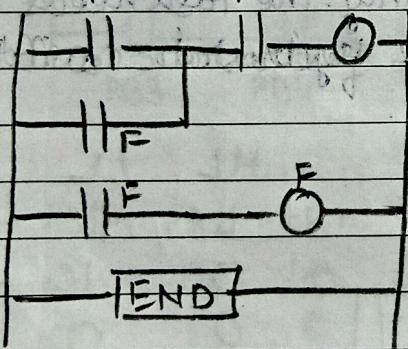


Tank is filled motor  
should stop.


• Logic

$$(A \bar{X} + \bar{A} X) (B \bar{Y} + \bar{B} Y) = Y$$


① AND

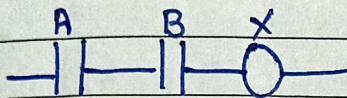

LD A  
AND B  
OUT X

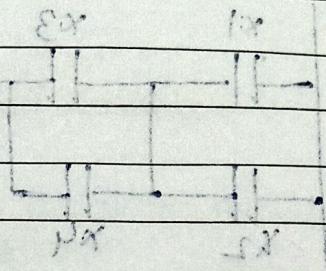


② OR

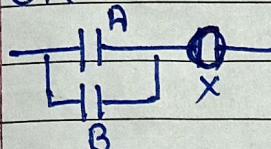


LD A  
OR B  
OUT X


③ XOR

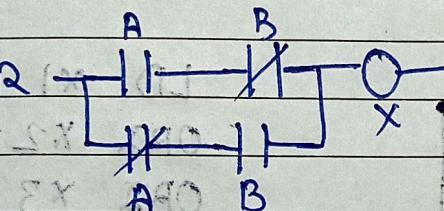
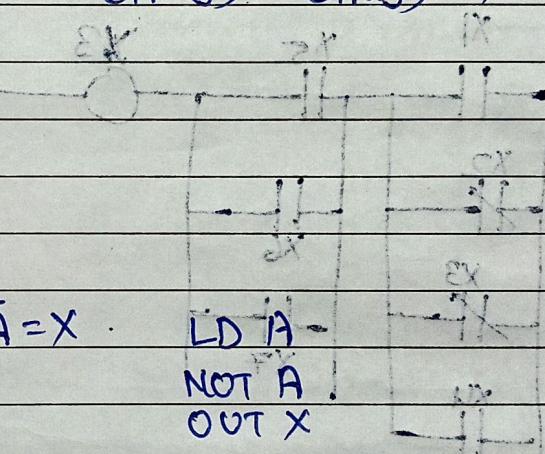
$$(A \cdot \bar{B}) + (\bar{A} \cdot B) = X$$




④ NOT

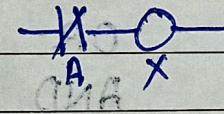

$\bar{A} = X$   
LD A  
NOT A  
OUT X


•  $Y = (X_1 \cdot X_2) + X_3$

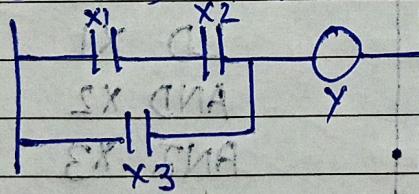


EX 6.11 OR GATE

EX 6.12 AND GATE

•  $Y = (X_1 + X_2) \cdot X_3$

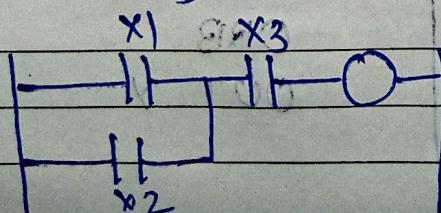

$$\bullet Y = (X_1 + X_2)(X_3 + X_4)$$

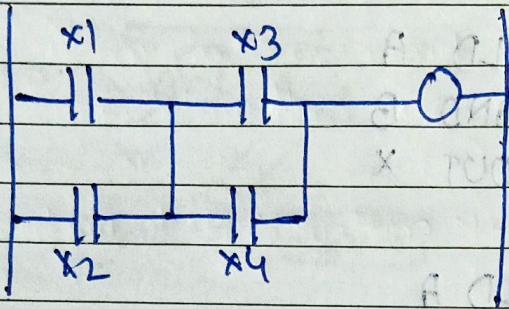

F C1

B RA


X T00

AND ①

OR ②


OR ③
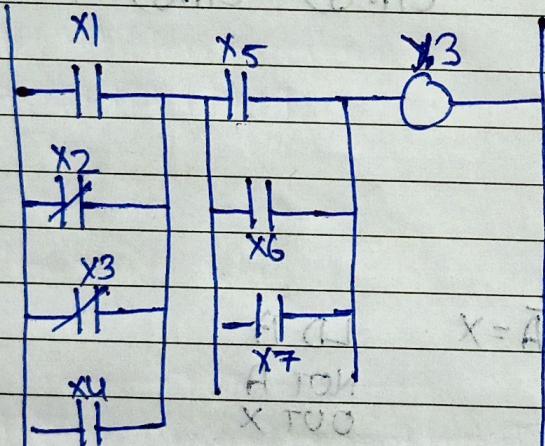
$$\bullet X = (\bar{A} \cdot \bar{B}) + (\bar{A} \cdot A)$$




X = A

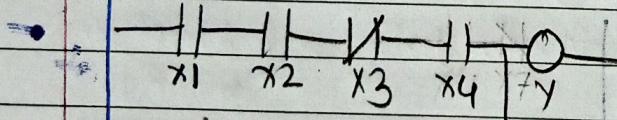LD X1  
 ORJ X2  
 ORJ X3  
 OR X4  
 LD X5  
 OR X6  
 OR X7  
 AND  
 OUT Y2



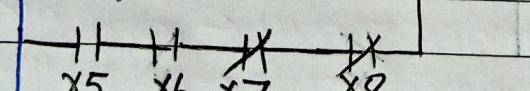LD X1  
 AND X2  
 AND X3  
 AND X4 ; LD X5  
 AND X6, AND X7  
 AND X8  
 ORB  
 OUT Y



LD X1  
 AND X2  
 AND X3  
 AND X4 ; LD X5  
 AND X6, AND X7  
 AND X8  
 ORB  
 OUT Y

## • PLC Mixer Process Controller Problem

X1 : Temperature Sensor

X2 : Pressure Sensor


X3 : Manual Switch/Push button


Manual Switch ON → Motor ON

Scan I/P from Temp, Pressure Sensors :

If both High → stop the motor.

Again manual switch → Motor OFF

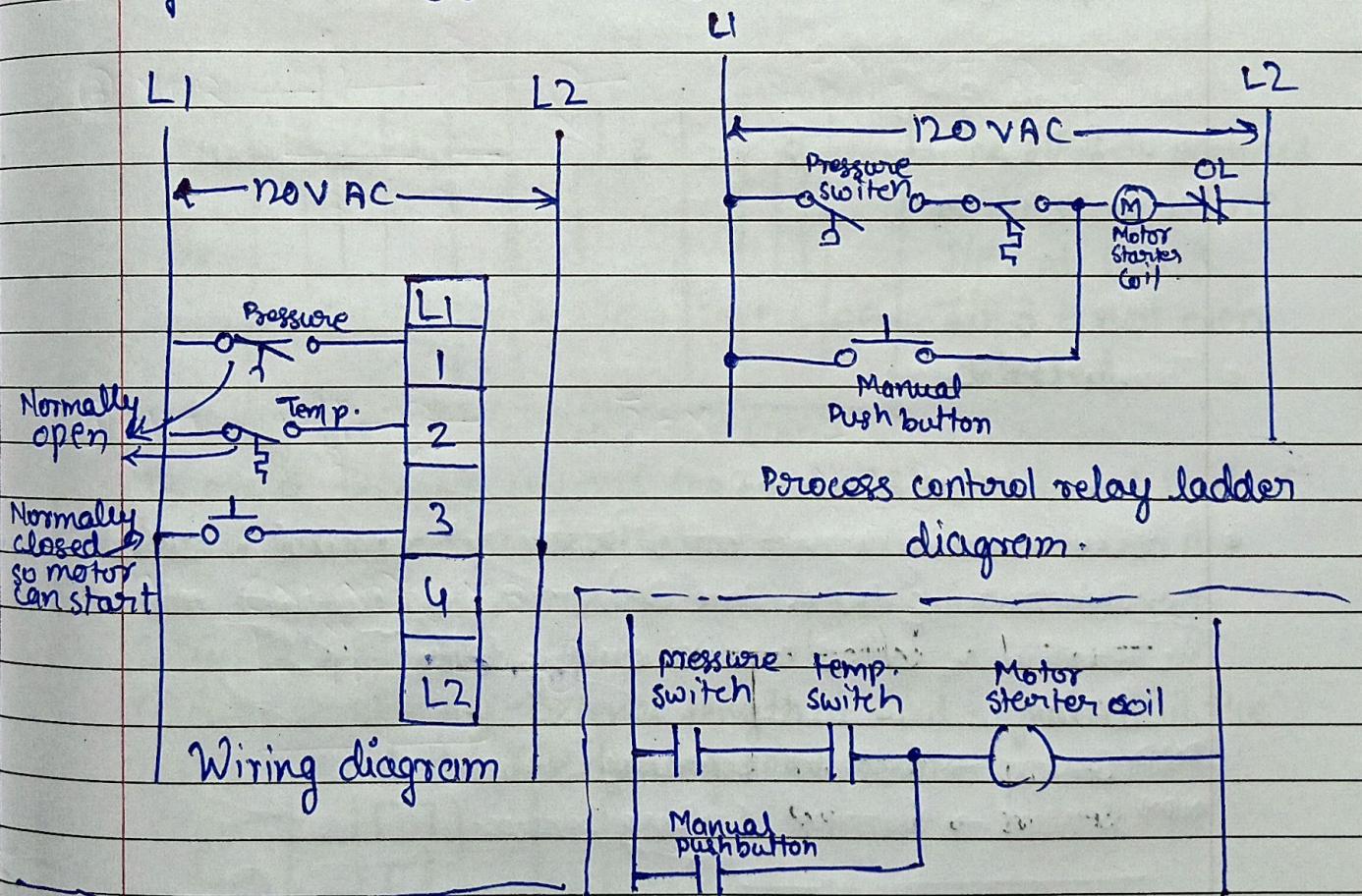

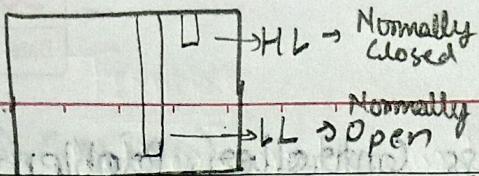


STOP

→ Always  
considered NC

NAMUR switches used in  
Hazardous areas



rotary limit switch closed (8) → 22mA

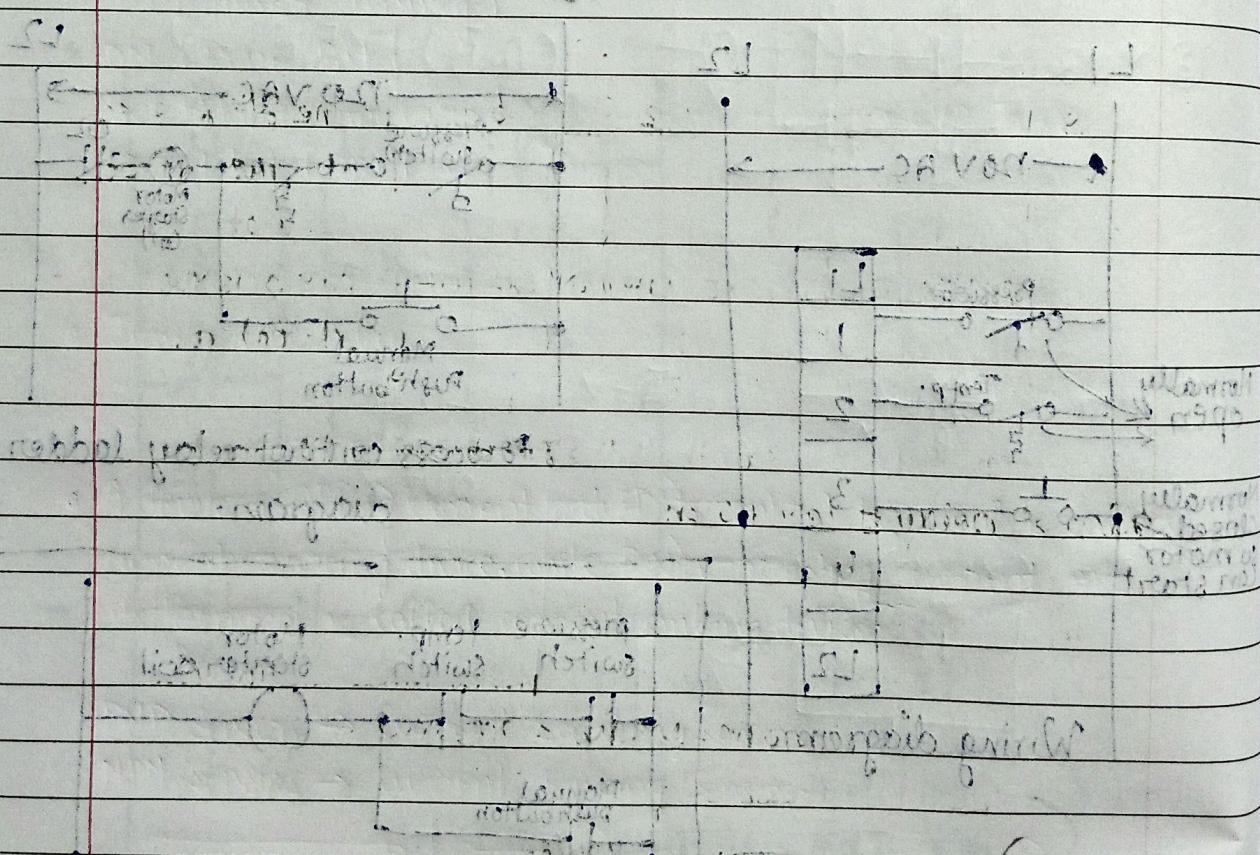400 volt 10A open 22mA 1mA  
• never exceed quiet mA 15mA  
• rotary limit switch damage (9) → 0mA  
70 micro ohms maximum rating



- How does PLC work?

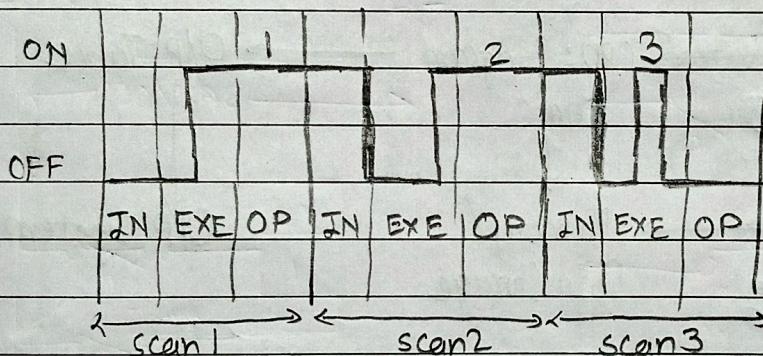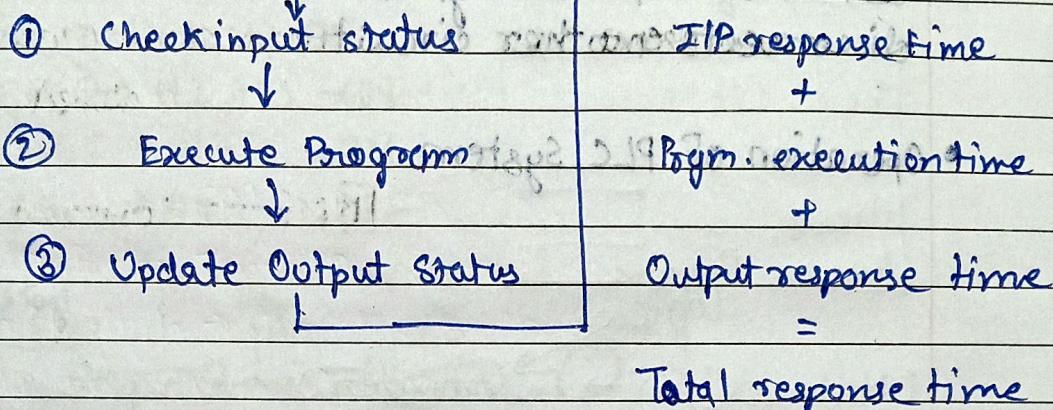PLC works by continuously scanning a program




The JIP 1 is scanned at time of Scan 2.  
JIP 2 at Scan 3.  
JIP 3 is not even detected.


To avoid this we say that the JIP should be ON for at least 2 input delay time + 2 scan.

In Techniques:-

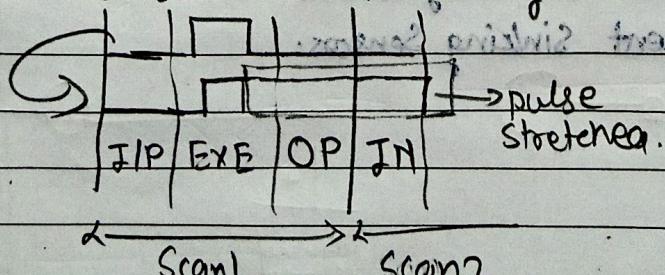
- Pulse Stretching - Extend length of input signal until the PLC looks at the JIP during next scan.



- Interrupt

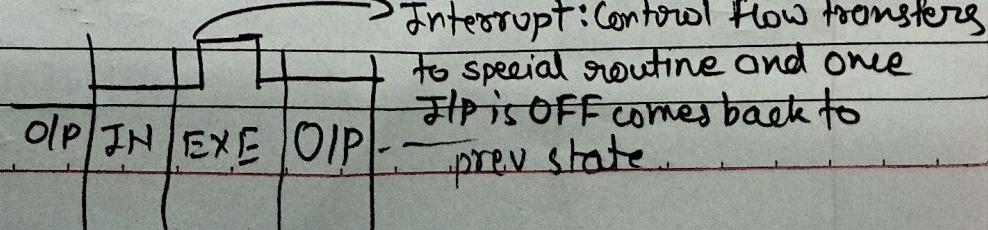

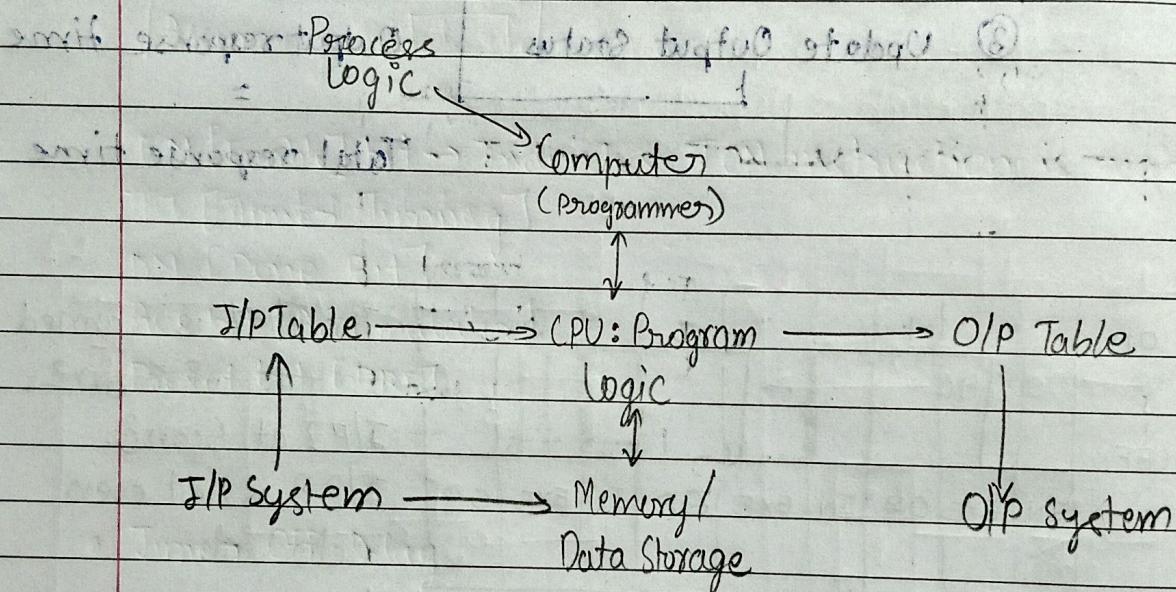- Relays [as electromagnetic switch].  
Uses an electromagnet; an electric signal to control an electromagnet which in turns connect or disconnects another circuit.
- Operation of PLC System



- A device sending current out of its control terminal is called current sourcing device, while device accepting current into its terminal is called current sinking device.

PNP Sensors → Current Sourcing Sensors.

NPN Sensors → Current Sinking Sensors.

Sinking

Sourcing

## LADDER DIAGRAMS




- ① To develop a ladder diagram for ON/OFF temperature controller for continuous process of heating of mixture

Temp < 55 → H1, H2, H3 ON

55 < Temp < 60 → H2, H3 ON


60 < Temp < 65 → H3 ON

Temp ≥ 65 → All OFF

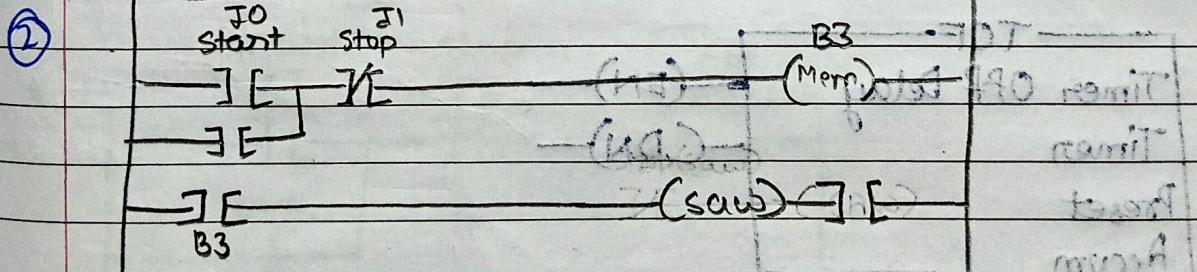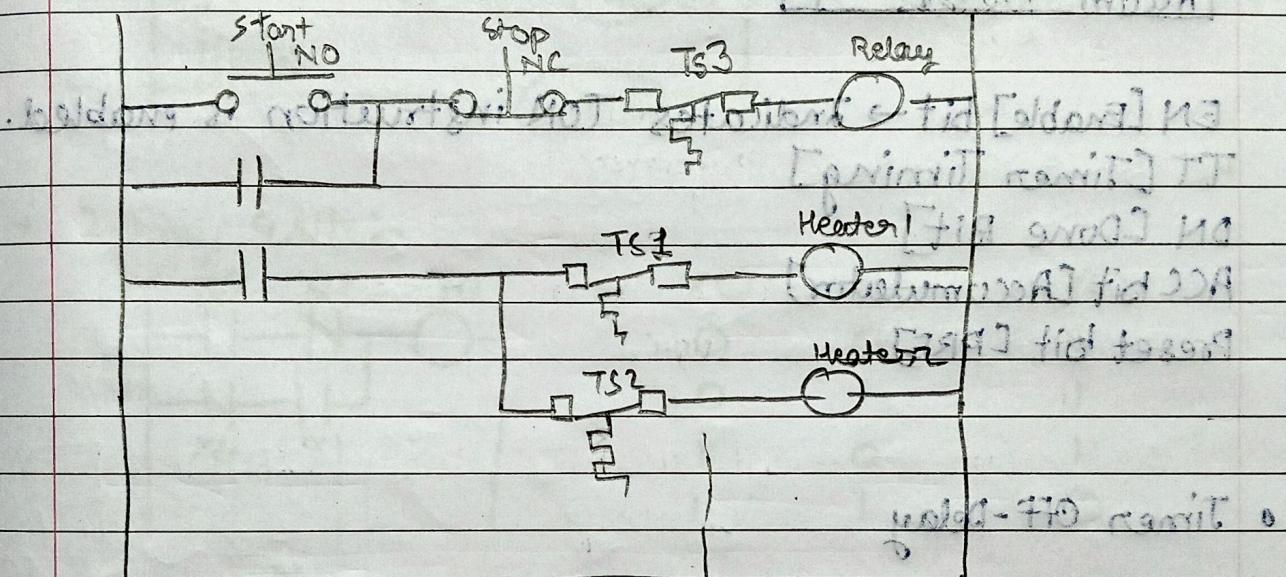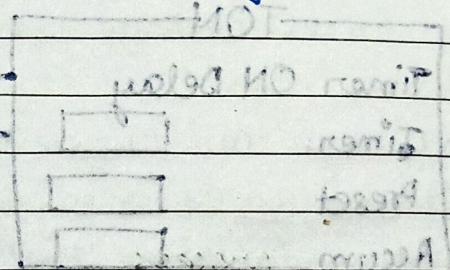

## TIMERS

- Timer On-Delay

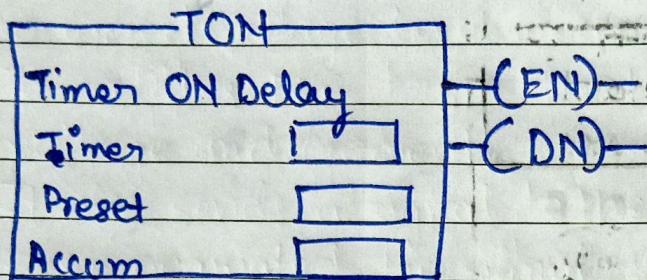

EN [Enable] bit → Indicates TON instruction is enabled.


TT [Timer Timing]

DN [Done Bit]

ACC bit [Accumulator]


Preset bit [PRE]

- Timer OFF-Delay

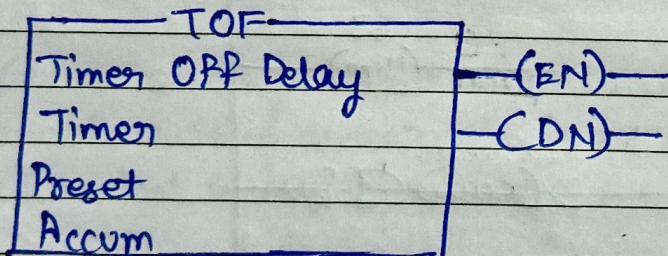


## • Deadman Switch

alibiM targets

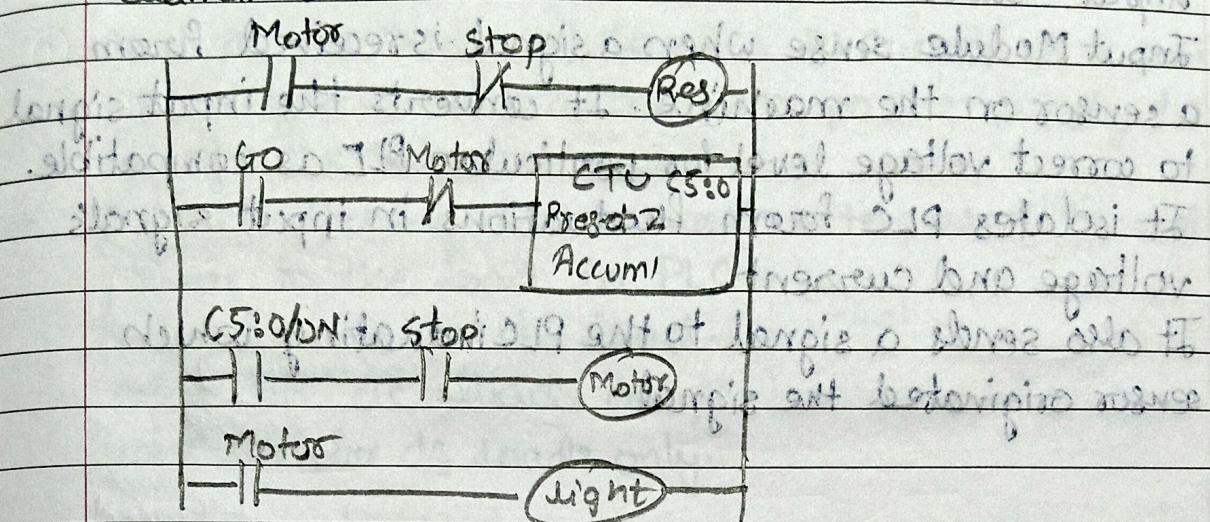


alibiM targets 38

## • 2-Way Switch

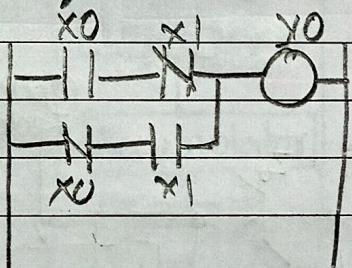

X0	X1	YO
0	0	0
0	1	1
1	0	1
1	1	0

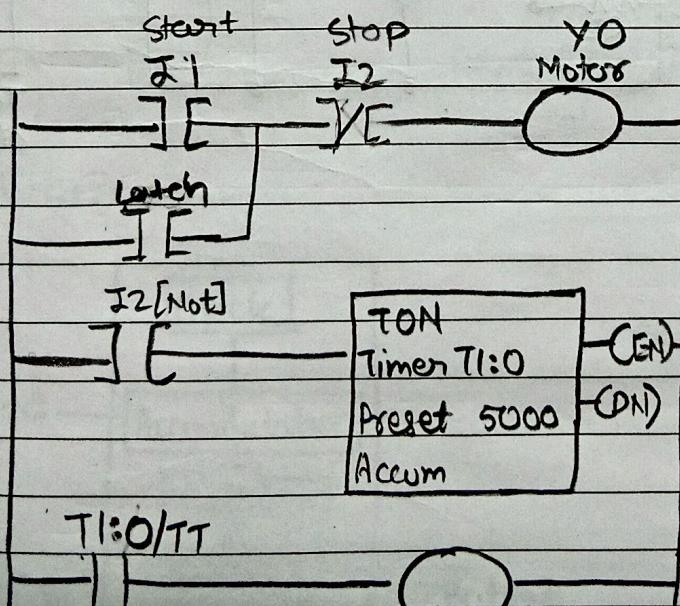


- **Input Module**

Input Module sense when a signal is received from a sensor on the machine. It converts the input signal to correct voltage level for particular PLC as compatible. It isolates PLC from fluctuations in input signal's voltage and current.

It also sends a signal to the PLC indicating which sensor originated the signal.

### AC Input Module

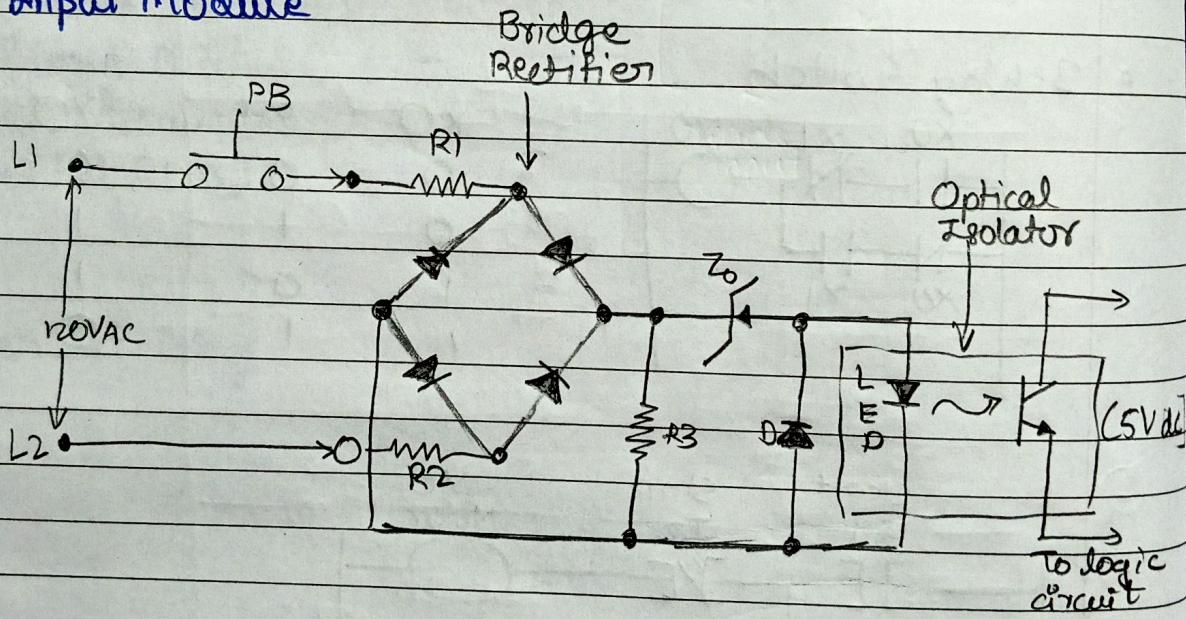

## • Output Module

Output interface module of a PLC acts as a switch to supply power from the user power supply to operate the output.


Output switching devices most often used to switch power to the load in PLC.

Relay for ac or dc load.


Transistor for ac loads only.

Transistors for dc loads only.


## • Counter

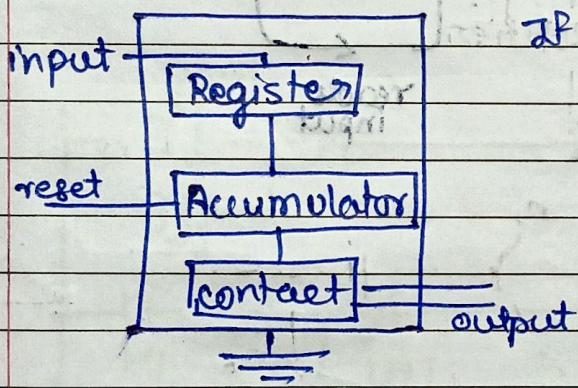



If counting till 5, then output


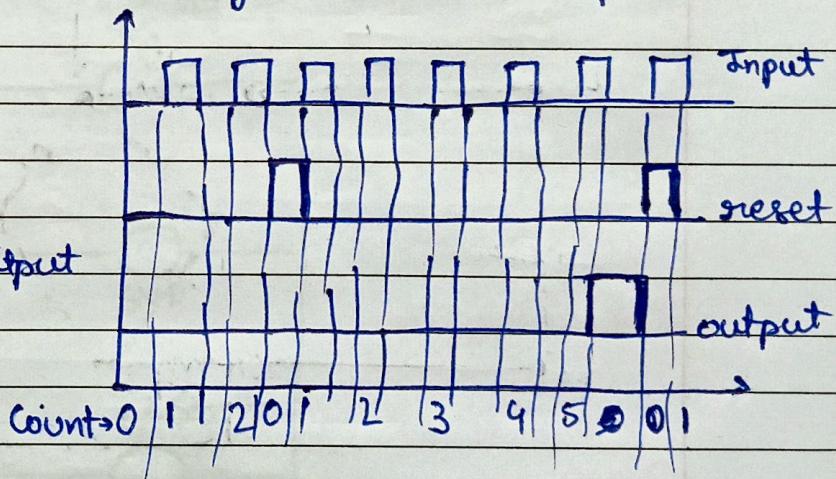



## • Timer

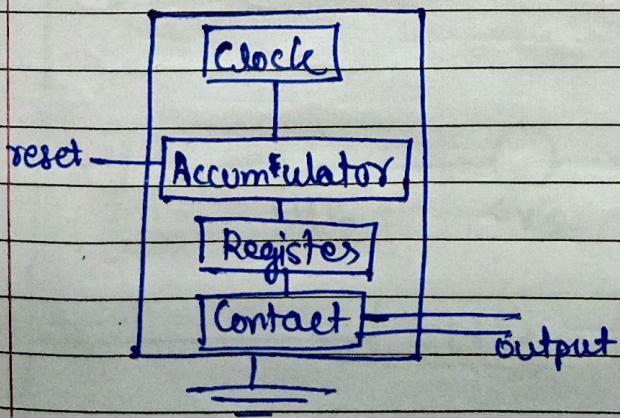

## PLC Scanning of Ladder Program

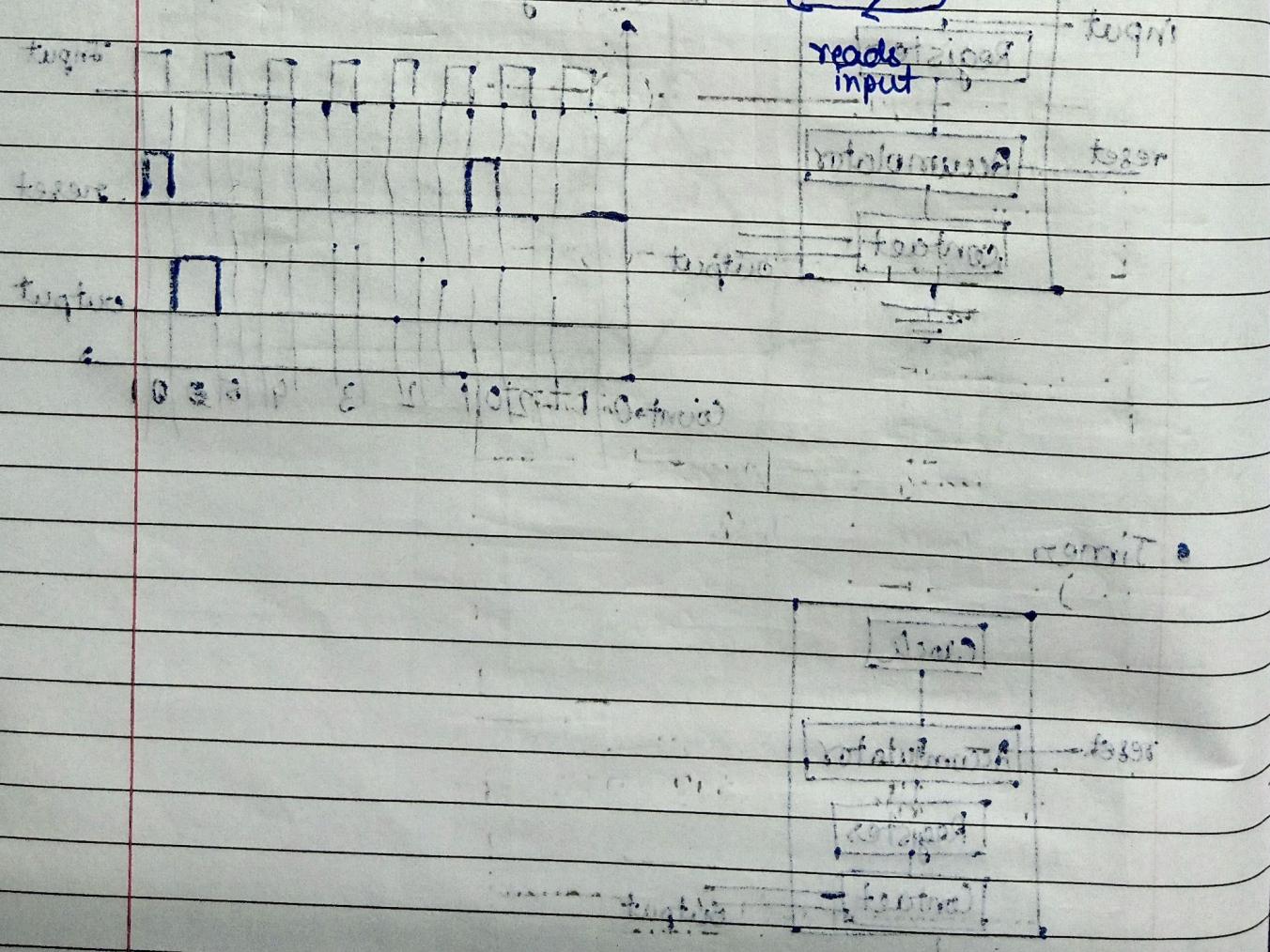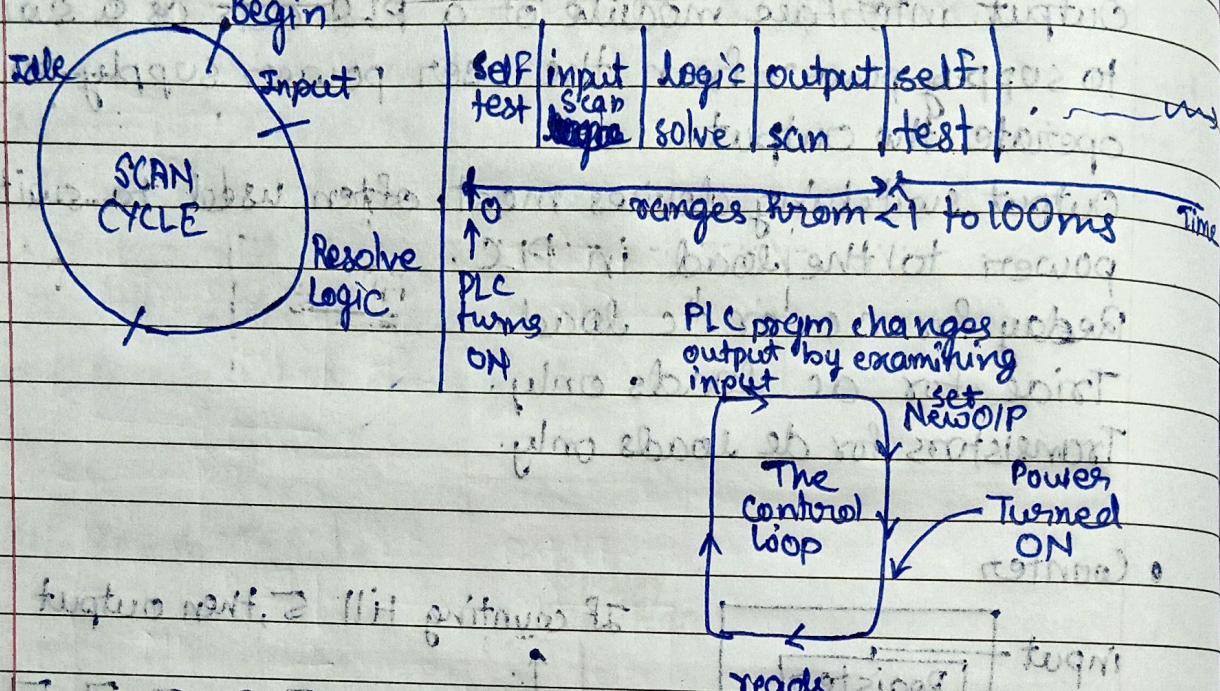


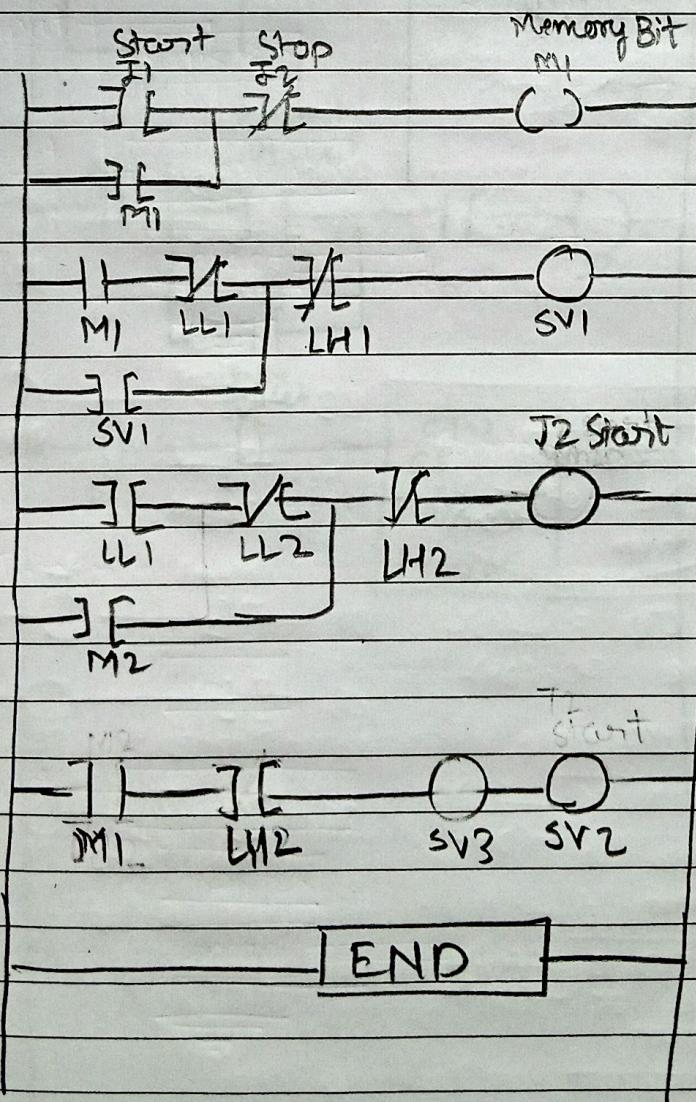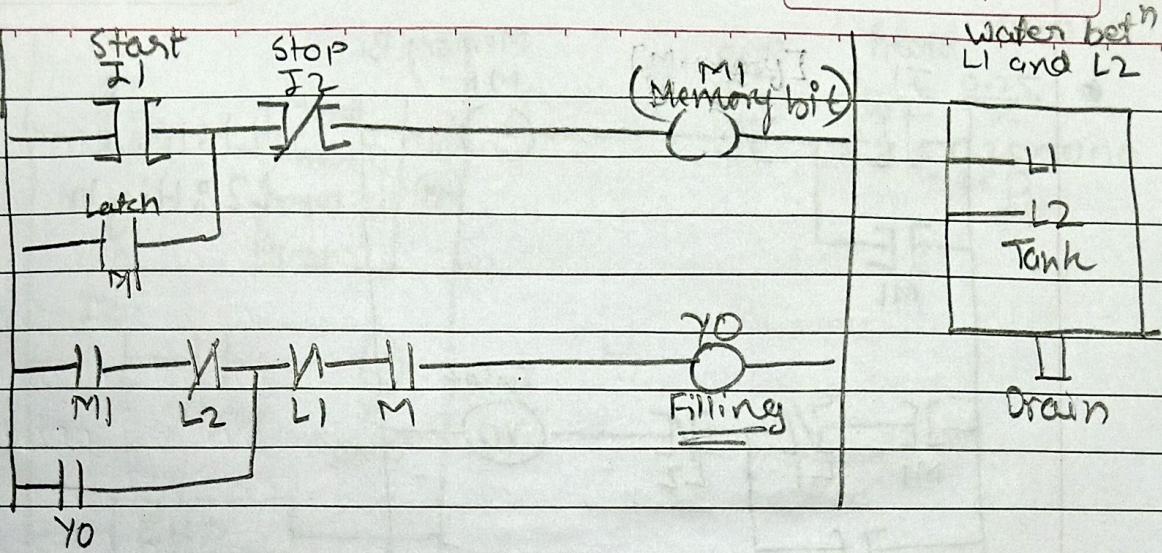

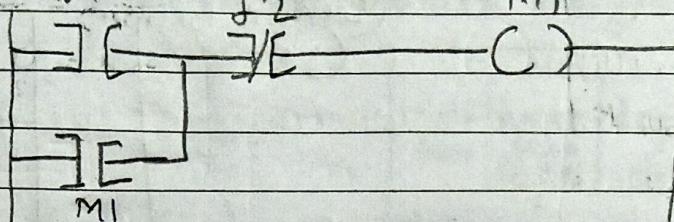
Start  
I1STOP  
J2Memory Bit  
M1

L1: low

L2: High

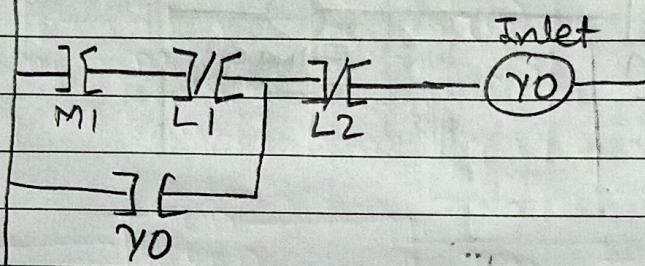



Inlet


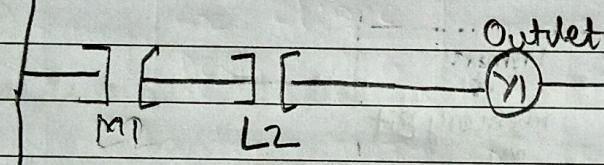


Outlet

$$1 \text{ sec} = 1000$$
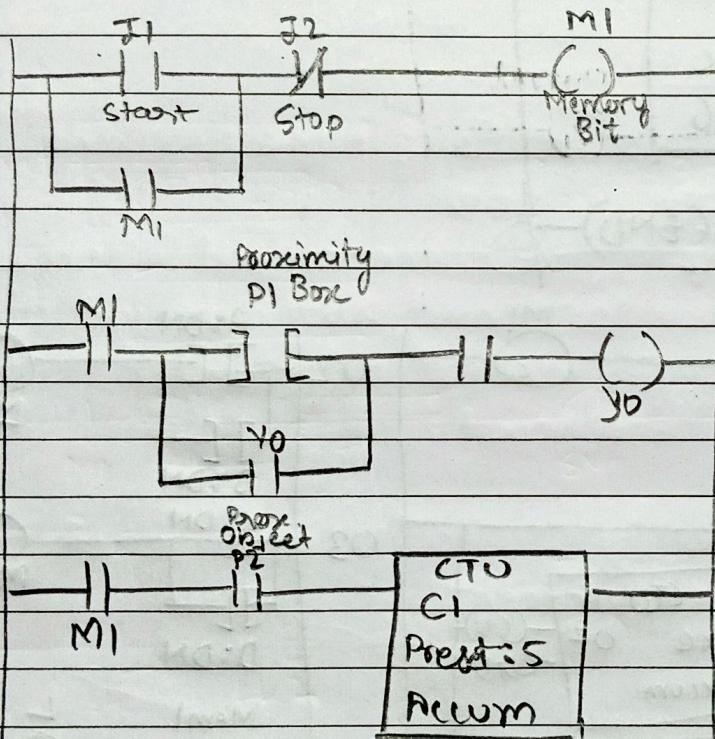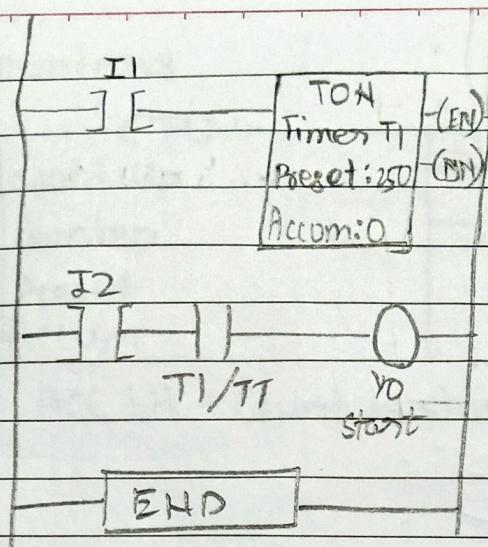
$$\begin{aligned}\frac{1}{1000} &= \frac{0.25}{x}, \\ \therefore x &= 0.25 \times 1000 \\ &= 250\end{aligned}$$



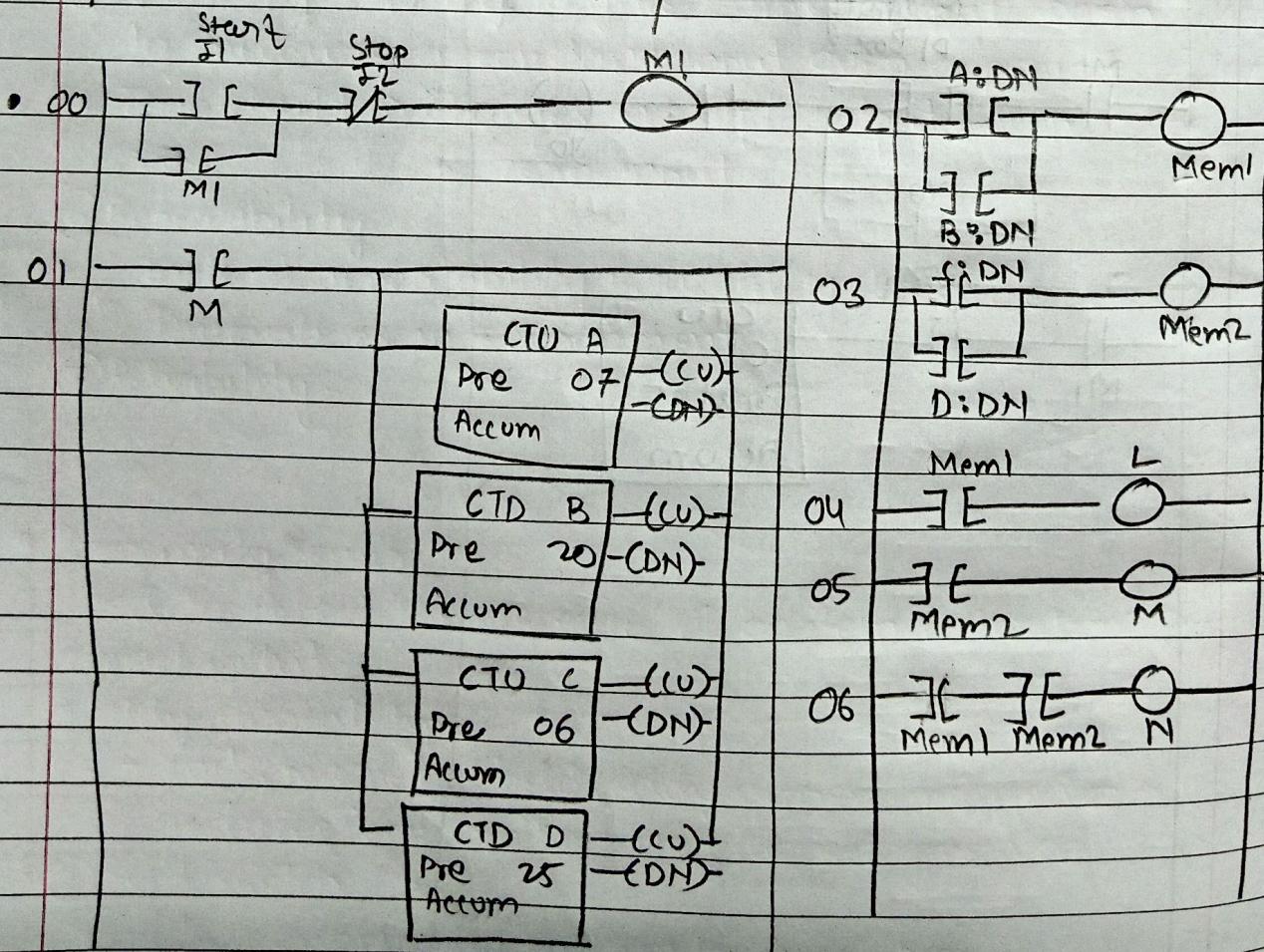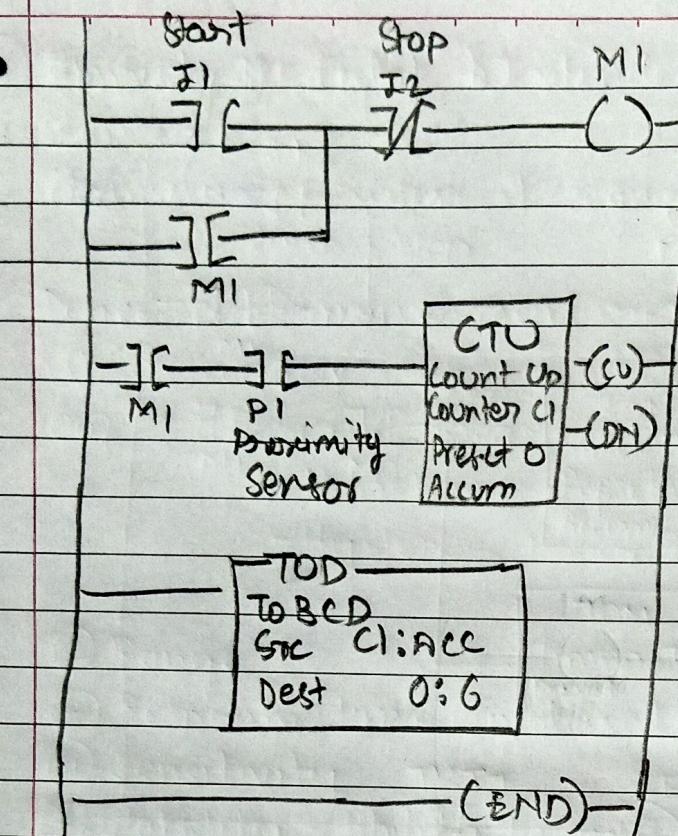

continued

## • Counters:

CTU  
Count Up  
Counter  
Preset  
Accum





(CU)  
(DN)


} CU Bit, CD bit, DN bit  
OV Bit, UN bit  
Preset bit: It specifies val. that  
accumulate value should reach to  
set DN bit.

ACC bit → Count is stored.

- Blinking of light  $\rightarrow$  2 sec

+ 10 KOs, time (0 to 10 s)

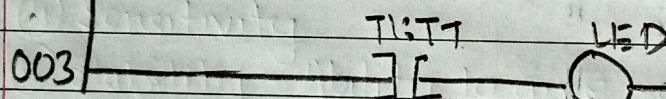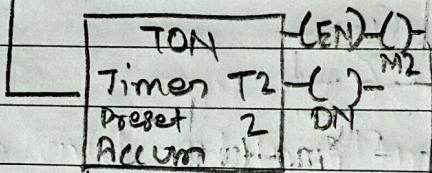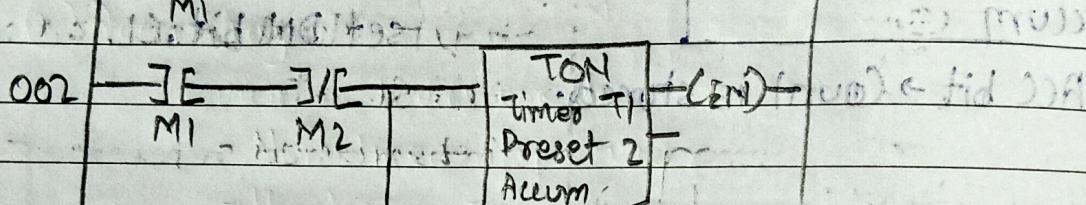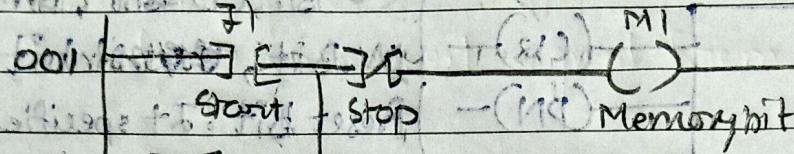

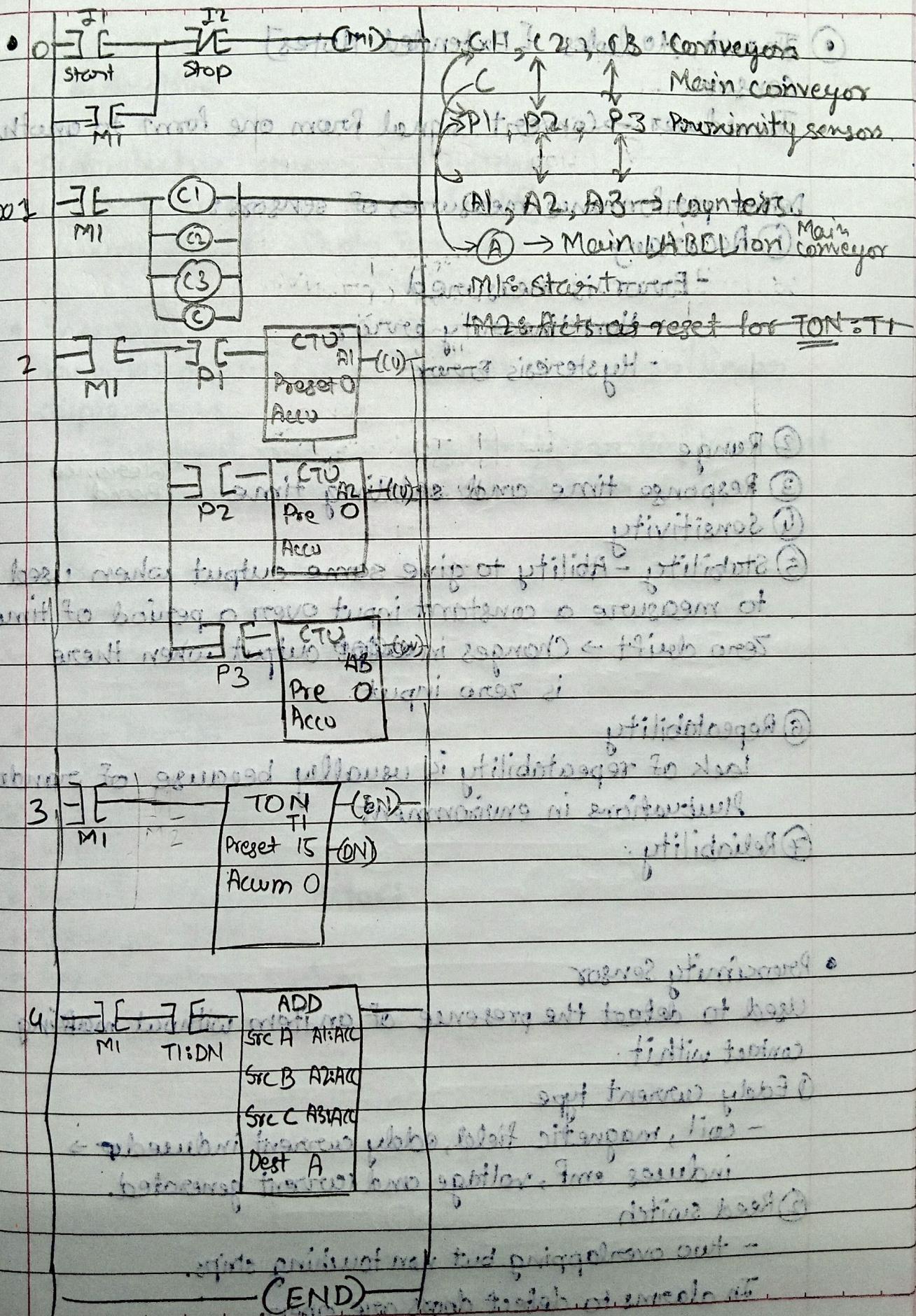

## ● Input Modules [Extended Notes]

### Sensor.

Transducer → Convert signal from one form to another.

Define performance measures of sensors:

#### ① Accuracy

- Error is measured
- Non-linearity error
- Hysteresis Error

#### ② Range

#### ③ Response time and settling time

Tolerance Band

#### ④ Sensitivity

#### ⑤ Stability - Ability to give same output when used to measure a constant input over a period of time.

Zero drift → Changes in ~~constant~~ output when there is zero input.

#### ⑥ Repeatability

Lack of repeatability is usually because of random fluctuations in environment

#### ⑦ Reliability.

### • Proximity Sensor

Used to detect the presence of an item without making contact with it.

#### ① Eddy current type

- coil, magnetic field, eddy current induced → induces emf, voltage and current generated.

#### ② Reed switch

- two overlapping but non touching strips.

In alarms to detect doors are open.

- ③ Capacitive
- ④ Inductive

- Photoelectric sensors and switches

Photo conductive Diode [cell]

Photodiode, Photo Transistor

- Encoders

Provides digital O/P as a result of angular/linear displacement.

Increment Encoder - angular/linear displacement

Absolute Encoder - angular/linear position

- Temperature Sensors

Bimetallic Strip [Coefficient of Expansion]

RTD [Resistive Temp. Detector]

- Strain Gauge

- Output Modules

- Relay

- Motors [Stepper Motor]


- Conveyor Belt

- Robot Control System

start STOP  
J1 J2

Memory Bit

Mb

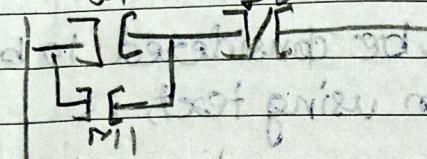


start button (J1) and stop button (J2) connected in parallel. M1 coil is energized.

Memory bit Mb is set during start and reset during stop.

Mb is reset after power supply is applied or if power fails.

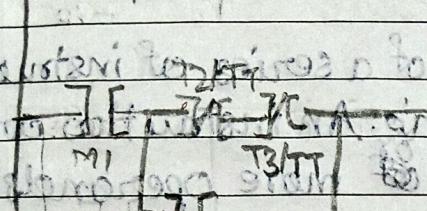Mb is set again when power is applied or if power fails.



TON : T1


(EN)

Preset 200

(CDN)

Accum

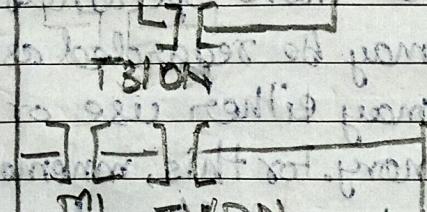Accumulator is initialized to preset value.



TON : T2


(EN)

Preset 100

(CDN)


Accum

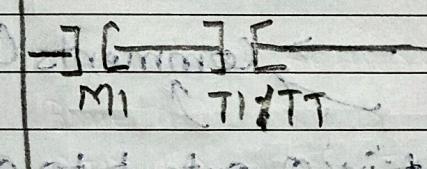Accumulator is initialized to preset value.



C1


C1A

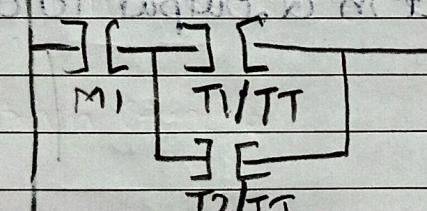

T2

T2A

Motor 2 : SMALLER

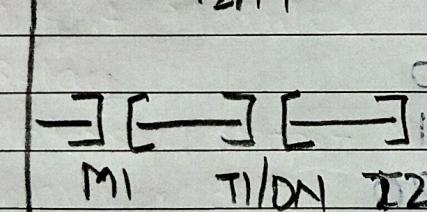

C00X C1

TON-T3


(EN)

Reset = 50

(CDN)

Accum

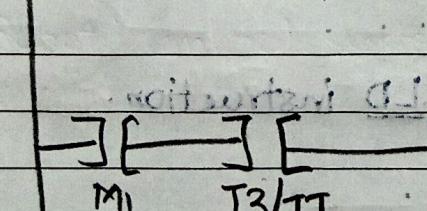Accumulator is initialized to preset value.



A C1

Motor 3

A C1A

S1

S2

S3

S256

## ● Instruction List


Programming method, which can be considered to be the entering of a ladder program using text, is Instruction List [IL].

IL gives programs which consists of a series of instructions, each instruction begins on new line. An instruction consists of an operator followed by one or more operands.


In terms of ladder, an operator may be regarded as ladder element. Each instruction may either use or change the values stored in memory. For this, mnemonic codes are used, each corresponding to an ladder element. It differs from manufacturer to manufacturer.


LD	A	(* Load A *)	→ Comments (* *)
AND	B	(* AND B *)	↓
ST	Q	(* STORE result in Q, output to Q *)	

LABEL NAME : - - -  
\_\_\_\_\_

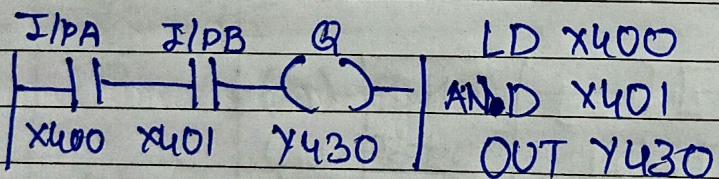

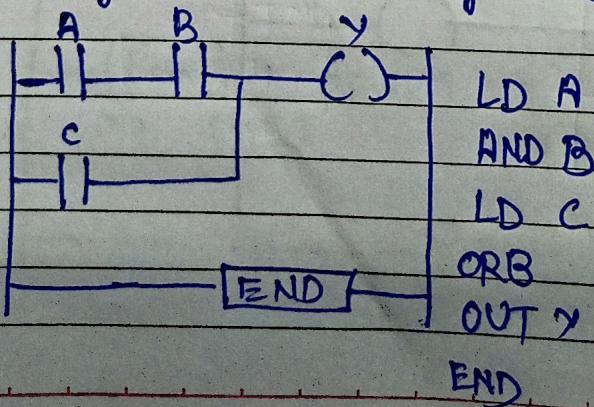Adding one more rung : Used LD instruction.



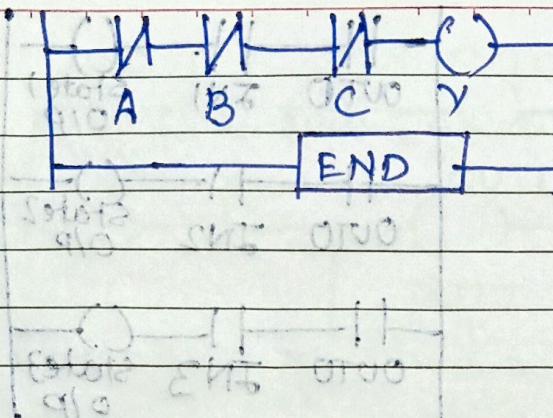

LDJ p. A (dancer's girl) •

ANI B


ANT C

OUT STUFF

END
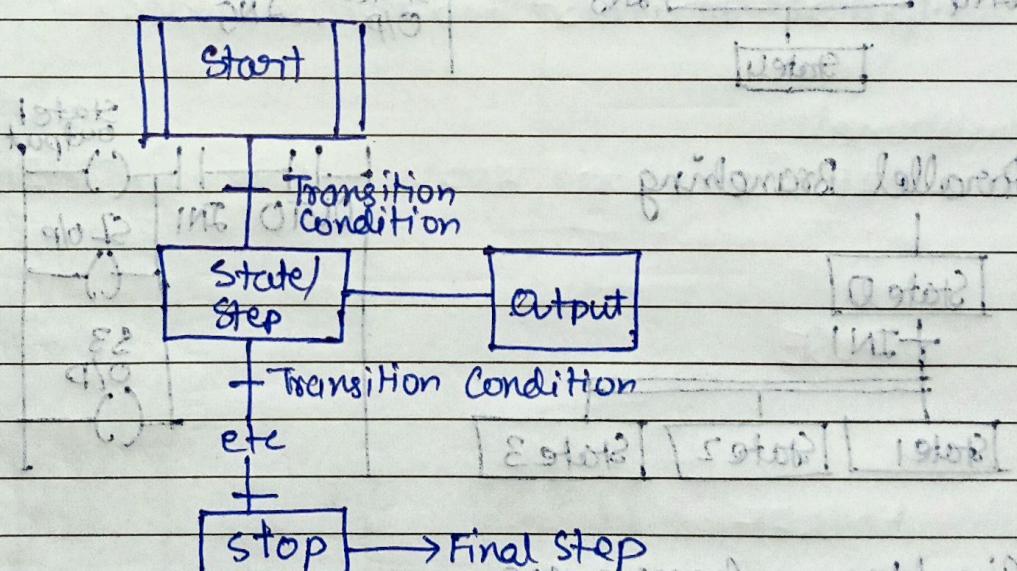
## ① Sequential Function Charts

It is used for pictorial representation of a system's operation to show the sequence of events in its operation.





*friderici fallax* •



Laotian  
Lao

19452



[Contact Us](#)

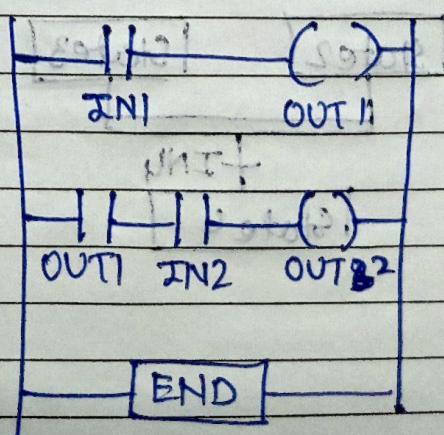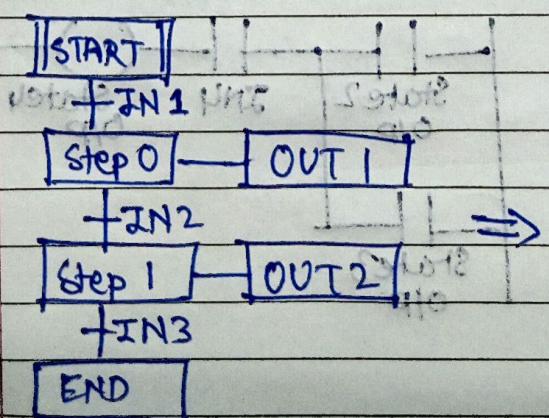



### Selective Branching

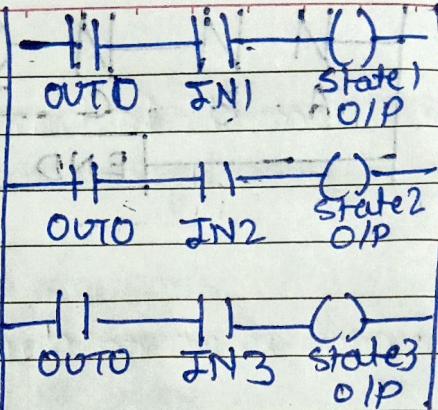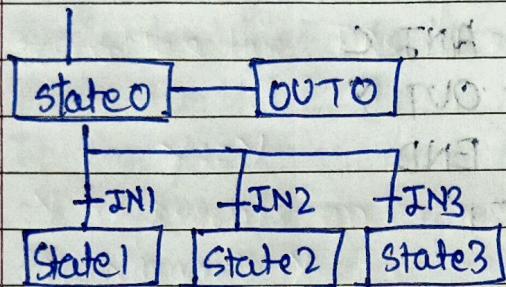



### Regressive Branching (Convergence)

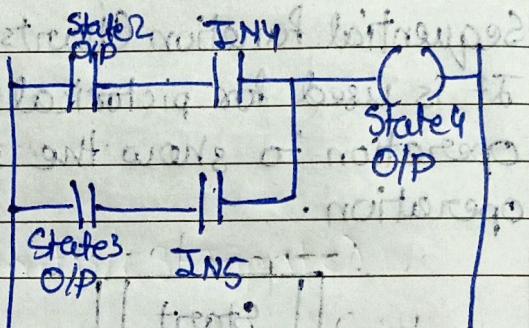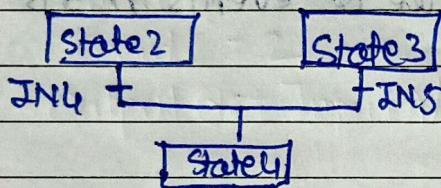


### Parallel Branching

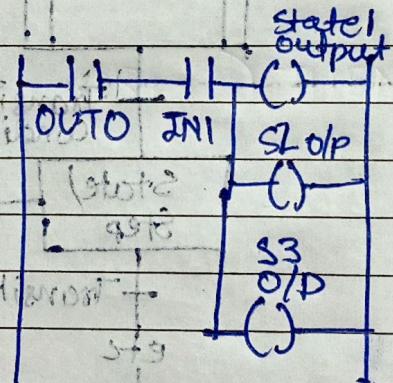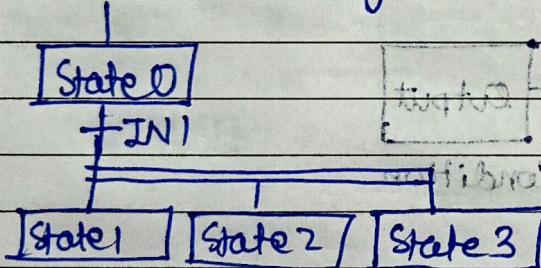

### Simultaneous Convergence

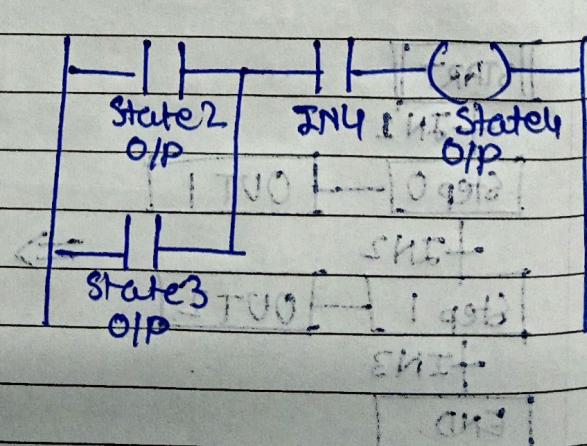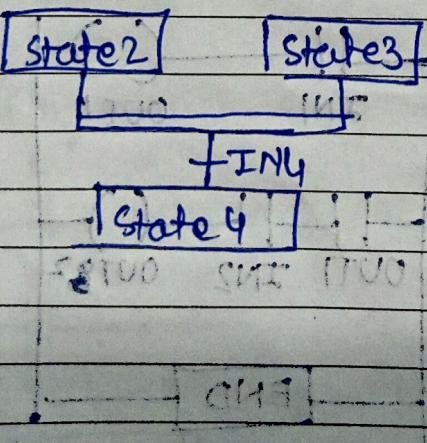

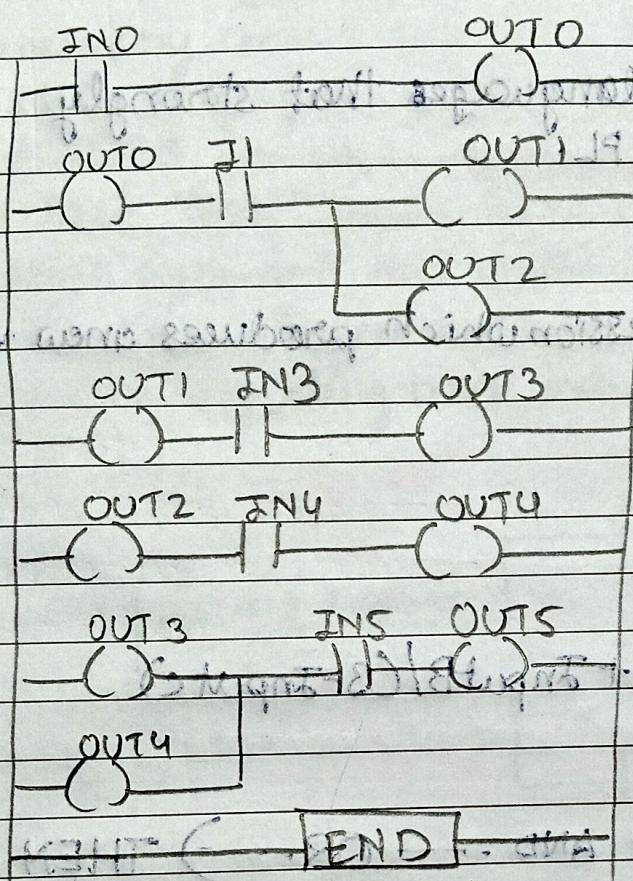

first has two inputs •

$V = X$

$X$  address of

$A = A$  input

$B = B$  input

$S = S$  input


$S = S$  output =  $A$  output

parallelism

(initial) 75

END

## • Actions

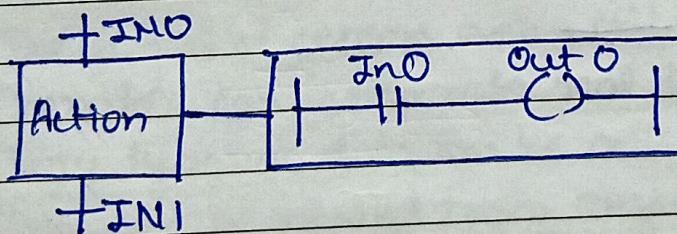

END

- Structured Text

It is a programming language that strongly resembles the PASCAL PL.

$X := Y$

$Y$  represents an expression which produces a new value for variable  $X$ .

Input A = 6

Input B = 4

Input C = 2


Output Q := InputA/3 + InputB/(3 - InputC)

Conditional:

IF (Condition) AND --- OR --- THEN


ELSE

END IF

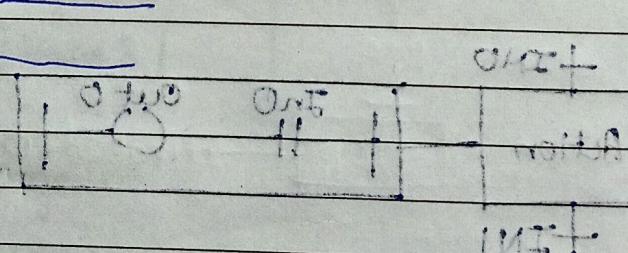
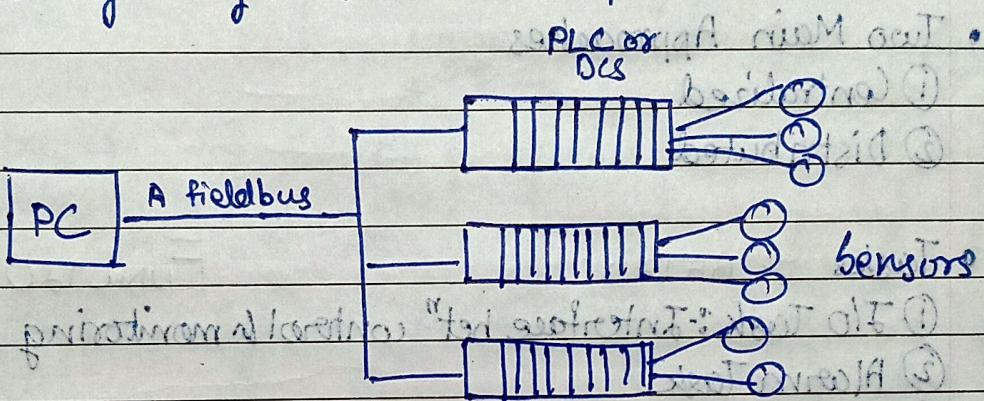
## SCADA

Supervisory Control and Data Acquisition (SCADA) is a system that is used for controlling industrial processes. It is a category of software applications for controlling industrial processes, which is the gathering of data in Real Time from remote location in order to control equipment and conditions. SCADA provides organization with tools needed to make and deploy data-driven decisions regarding their industrial processes.



### Advantages :-

- ① Computers can record and store a very large amount of data.
- ② Data can be used for analytics and forecast provide better view.
- ③ Thousands of sensors over a wide area can be connected.
- ④ Operator can incorporate real data simulations.
- ⑤ Many types of data can be collected from RTUs.
- ⑥ Data can be viewed from anywhere.

### Disadvantages:-

- ① System is more complicated.
- ② Different Operating skills are required.
- ③ With lots of sensors, a lots of wire to deal with.
- ④ Operators can see only as far as the PLC.

ACADEMIC

- SCADA Hardware
  - ① Field level instrumentation and control devices.
  - ② Marshalling terminals and RTUs
  - ③ Communication Systems
  - ④ Master station(s)
  - ⑤ Commercial data processing dept. computer system

- Two Main Approaches

- ① Centralized

- ② Distributed

- Tasks → RTAD

- ① I/O Task :- Interface bet" control & monitoring sys. and plant
- ② Alarm Task
- ③ Trends Task :- Collect data to be monitored over time.
- ④ Reports Task :-
- ⑤ Display Task :- Manages all data to be monitored and activated by all control actions requested by operator

## FUNCTIONS

- Key Features

- ① User Interface with user management and reporting
- ② Graphics Display allows at most 3D object visualisation
- ③ Alarms - Detectors most frequently used include
- ④ Trends
- ⑤ RTU and PLC interface
- ⑥ Scalability
- ⑦ Access to database and clients publishing information
- ⑧ Database - gives the ability to store large amounts of data efficiently
- ⑨ Networking - to send and receive data and information
- ⑩ Fault Tolerance and Redundancy
- ⑪ Client/server distributed processing

ACADEMIC

- SCADA Hardware
  - ① Field level instrumentation and control devices.
  - ② Marhsalling terminals and RTUs
  - ③ Communication Systems
  - ④ Master station(s)
  - ⑤ Commercial data processing dept. computer system

- Two Main Approaches

- ① Centralized

- ② Distributed

- Tasks → RTAD

- ① I/O Task :- Interface bet" control & monitoring sys. and plan
  - ② Alarm Task
  - ③ Trends Task :- Collect data to be monitored over time.
  - ④ Reports Task :-
  - ⑤ Display Task :- Manages all data to be monitored and achieves "local" control actions requested by operator


exhibit A

## FUNCTIONS

- Key Features

- ① User Interface
  - ② Graphics
  - ③ Alarms
  - ④ Trends
  - ⑤ RTU and PLC interface
  - ⑥ Scalability
  - ⑦ Access to data
  - ⑧ Database
  - ⑨ Networking
  - ⑩ Fault Tolerance and Redundancy
  - ⑪ Client/server distributed processing

- Layers of SCADA System Architecture

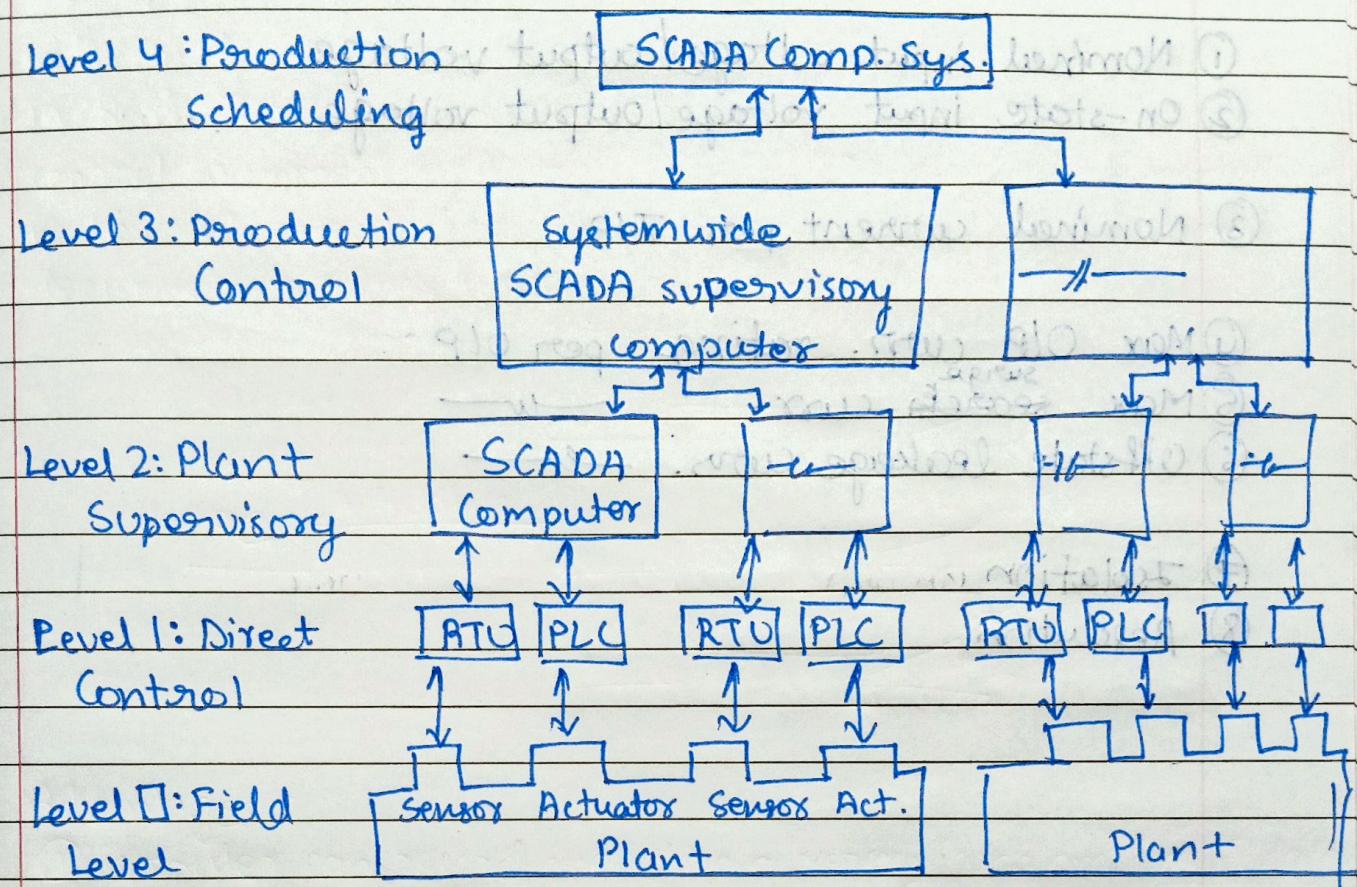

- Applications

- ① Electricity generation to distribution
- ② Oil and Gas refining operation
- ③ Telecommunication infrastructure
- ④ Chemical Manufacturing